 


## Applications of State Machines

**Exercise 1:** The example above is an N-bit shift register that shifts the bits right. Draw a block diagram and write the Verilog for a 6-bit shift register that shifts left.

### Exercise 2:



Fill in the diagram above for a 4-bit ( $N = 4$ ) right-shift shift register. Assume the initial value is zero. Which bit is the oldest (first) value in the waveform? Which bit of the shift register holds the oldest value?

**Exercise 3:** Draw a block diagram and write the Verilog for a circuit that sets an output named **detect** high when the sequence of values 1, 1, 0, 1 has appeared on an input named **in** on successive rising edges of the clock.

**Exercise 4:** How could you modify the code so that **digits** is only updated when an **enable** input is asserted?

**Exercise 5:** How many states can this state machine have?

**Exercise 6:** Draw the state transition diagram for this simpler implementation. How many states are there? Write the Verilog using a 3-bit **count** state variable.

**Exercise 7:** For which states would a **fell** output be asserted? A **rose** output? Draw the schematic and write the Verilog for this state machine. Assume an input **in** and a 2-bit register **bits** that holds the two most recent input values.

**Exercise 8:** Can you design an edge detector that uses only one bit?  
Is this a Mealy or a Moore state machine?



**Exercise 9:** Write `always_ff` statements that implement these state machines.

**Exercise 10:** Write the state transition table for this state machine.