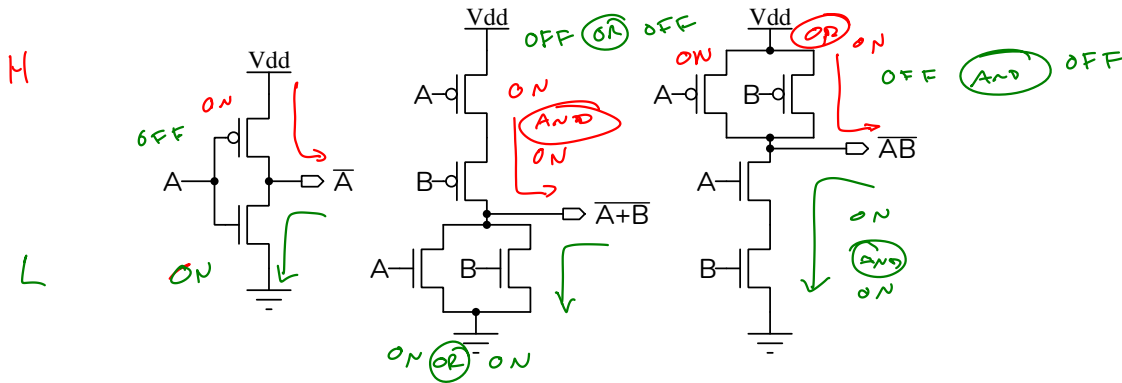


Implementation of Digital Logic Circuits

Exercise 1:



In which direction does the output current flow when the output is high? When it is low? Which transistors are on in each case?

H output: current out

L output: current in


H output: top on bottom off

L output: top off bottom on

on: ALL series transistors on
ANY parallel " on

off: ANY series transistors on
ALL parallel " off


Exercise 2:

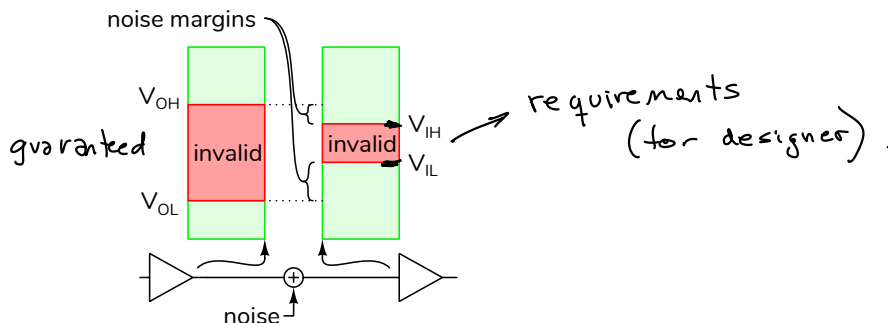

Which of these specifications does the manufacturer guarantee?

Which are requirements?

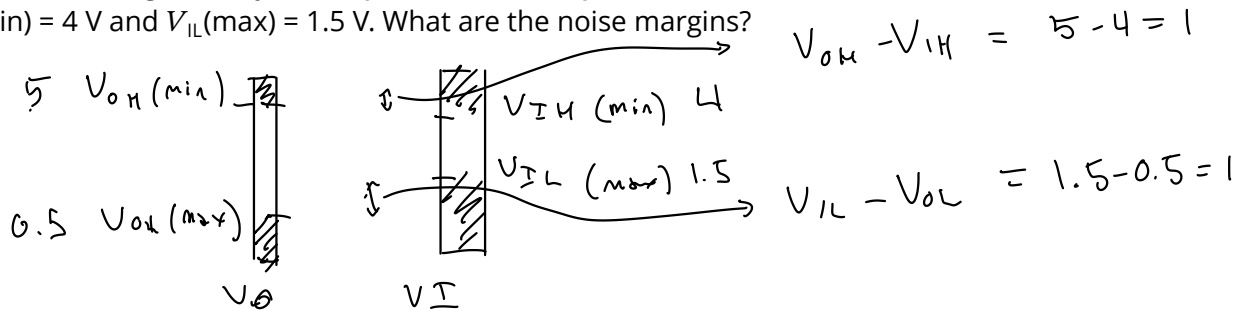Exercise 3: A logic family has $V_{OH(min)} = 5\text{ V}$, $V_{OL(max)} = 0.5\text{ V}$, $V_{IH(min)} = 4\text{ V}$ and $V_{IL(max)} = 1.5\text{ V}$. What are the noise margins?



Exercise 4: All else being equal, by how much would we expect to decrease power consumption when reducing logic levels from 5 V to 3.3 V? What would be the effect on power consumption in reducing the clock frequency from 50 MHz to 1 MHz?


$$V_1 = 5, V_2 = 3.3, \frac{P_2}{P_1} = \left(\frac{3.3}{5}\right)^2 \approx 0.44, P_2 = 0.44 P_1$$

$$f_1 = 50, f_2 = 1, \frac{P_2}{P_1} = \frac{1}{50} = 0.02, P_2 = 0.02 P_1$$

$$\text{reduction} = P_1 - P_2 = (1 - 0.44)P_1 = 0.56 P_1 = 56\% \text{ of } P_1$$

$$\text{reduction} = P_1 - P_2 = (1 - 0.02)P_1 = 0.98 P_1 = 98\% \text{ of } P_1$$

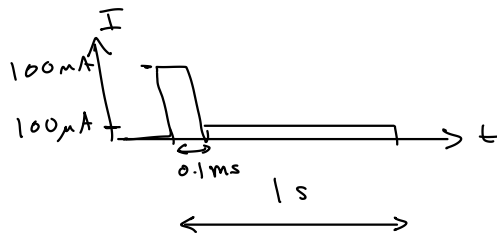Exercise 5: The energy stored in a battery (its "capacity") is measured in Watt-hours. If a circuit draws 100 mA for 100 μs per second and draws 100 μA the rest of the time, how long will a 1000 mAh battery last?



$$\text{Average current} = \frac{0.1 \times 10^{-3}}{1} 100 + \frac{(1 - 0.1 \times 10^{-3})}{1} 100 \times 10^{-3} \text{ mA}$$


$$\approx 10 \times 10^{-3} + 100 \times 10^{-3} - 10 \times 10^{-6}$$

$$\approx 110 \times 10^{-3} \text{ mA} \approx 110 \mu\text{A}$$

$$1000 \text{ mA} \cdot \text{h} \cdot 3600 \text{ s/h} = 3.6 \times 10^6 \text{ mA} \cdot \text{s}$$

$$\text{time} = \frac{3.6 \times 10^6 \text{ mA} \cdot \text{s}}{0.110 \text{ mA}} \approx 32.7 \times 10^6 \text{ s} \approx 9000 \text{ hours} (\approx 1 \text{ year})$$

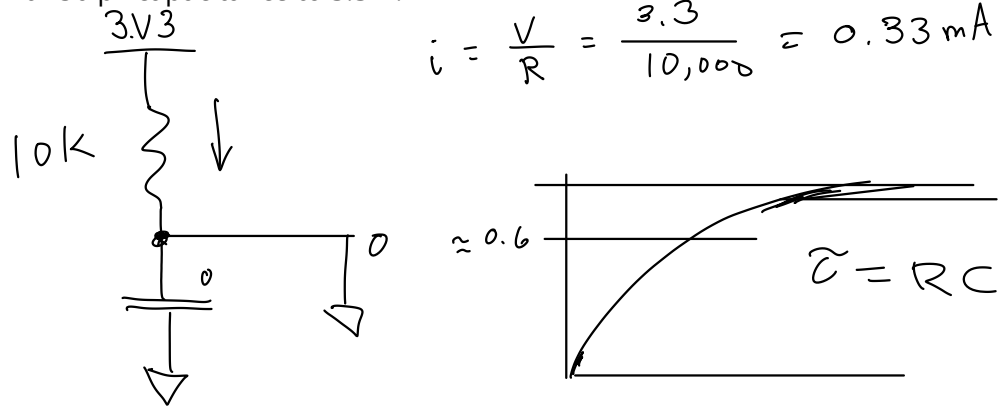Exercise 6: What are the active-state current and the RC time constant for a wired-or interrupt-request line using a 10kΩ resistor pulling up a circuit with 50 pF capacitance to 3.3 V?



$$i = \frac{V}{R} = \frac{3.3}{10,000} = 0.33 \text{ mA}$$

$$R = 10 \text{ k}\Omega$$

$$C = 50 \text{ pF}$$

$$\begin{aligned} \tau = RC &= 10 \times 10^3 \times 50 \times 10^{-12} \\ &= 500 \times 10^{-9} = 0.5 \mu\text{s}. \end{aligned}$$

Exercise 7: How many square mm of PCB area does each package require? Which packages have their pins accessible when the package is placed on the PCB?



$$\text{area} = \begin{cases} (22)^2 = 484 \\ (3.5)^2 = 12.25 \end{cases} \quad \nearrow \approx 40 \times$$