

Introduction to Digital Design with Verilog HDL

Exercise 1: What changes would result in a 3-input OR gate?

Exercise 2: What schematic would you expect if the statement was
`assign y = (a ^ b) | c ;?`

Exercise 3: If the signal **i** is declared as **logic [2:0] i;**, what is the 'width' of **i**?

If **i** has the value 6 (decimal), what is the value of **i[2]**?

Of **i[0]**?

Exercise 4: What are the widths and values, in decimal, of the following:

4' b1001?

5' d3?

6' h0_a?

3?

Exercise 5:

```
logic [3:0] z [0:1] = ' 3'b11, 3'b101 ;
```

Draw a two-dimensional table showing the values of the bits in **z**.

Exercise 6: Write the truth table for a one-bit adder with carry. There are three inputs (**a**, **b** and **carry**) and two outputs (**sum** and **carry**). Define an array that implements this function. Write an expression that uses this array to find the sum and carry of **logic** signals **a** and **b**.

Exercise 7: What are the values of the following expressions: `!4'b010`?

`~4'b010`?

`0+~(!0)`?

Exercise 8: An array declared as `logic [15:0] n;` and has the value `16'h1234`. What are the values and widths of the following expressions?

`n[15:13]`

`!n`

`~n[3:0]`

`n>>4`

`n + 1'b1`

`n[7:0] - n[3:0]`

`n >= 16'h1234`

`n ^ '1`

`n && !n`

`n * (!n + 1'b1)`

Exercise 9: What are the width and value of the expression: $3 \cdot 16' d10 : 8' h20$?

If x has the value 0, what is the value of the expression: $1'b1 : 1'b0$?

If x has the value -1?

Exercise 10: Draw the schematics corresponding to:

$y = a ? (b ? s1 : s2) : (c ? s3 : s4);$

$y = a ? s1 : b ? s2 : c ? s3 : s4;$

`y = a ? b ? c ? s3 : s4 : s2 : s1 ;`

Exercise 11: Use slicing and concatenation to compute the byte-swapped value of an array `n` declared as `logic [15:0] n`.

Exercise 12: If `n` has the value `16'h1234`, what are the value and width of:

`{n[7:0], n[15:8], 4'b1111}`?

Exercise 13: Use concatenation to shift n left by two bits.

Exercise 14: Use concatenation to assign the high-order byte of **n** to **a** and the low-order byte to **b**.


Exercise 15:

```
assign y = a + 1 ;
```

Some software warns about truncation. How could you re-write the **assign** statement to avoid such a warning?

Exercise 16: Write an `always_ff` statement that toggles (inverts) its one-bit output on each rising edge of the clock.

Exercise 17:

 

Identify the following in the diagram above: component names, component "instance names," component port names, module port names. Label the signal `t` in the schematic.

Exercise 18: Rewrite the **ex60** module using operators. Which version – “structural” or “behavioural” – is easier to understand?