

Introduction to Digital Design with Verilog HDL

Exercise 1: What changes would result in a 3-input OR gate?


```
// AND gate in Verilog

module ex1 ( input logic a, b, c,
             output logic y );

    assign y = a & b; a | b | c;

endmodule
```

Exercise 2: What schematic would you expect if the statement was `assign y = (a ^ b) | c ;`?

 

Exercise 3: If the signal `i` is declared as `logic [2:0] i;`, what is the 'width' of `i`?

3 bits

If `i` has the value 6 (decimal), what is the value of `i[2]`?

$$6_{10} = 110_2 \quad i = (1, 1, 0)$$

Of $i[0]$?

Exercise 4: What are the widths and values, in decimal, of the following:

	width	value (decimal)
4'b1001?	4	9
5'd3?	5	3
6'h0_a?	6	10
3?	32	3

Exercise 5:


logic [3:0] z [0:1] = ' 3'b11, 3'b101 ;

Draw a two-dimensional table showing the values of the bits in z.

0	0	1	1
0	1	0	1

Exercise 6: Write the truth table for a one-bit adder with carry. There are three inputs (**a**, **b** and **carry**) and two outputs (**sum** and **carry**). Define an array that implements this function. Write an expression that uses this array to find the sum and carry of **logic** signals **a** and **b**.

a	b	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

	sum	carry
00	0	0
01	1	0
10	1	0
11	0	1

`logic [1:0] tt [0:3] =`

`{ 2'b00, 2'b10, 2'b10, 2'b01 };`

`assign y = tt[{a,b}];`

Exercise 7: What are the values of the following expressions: `!4'b010?`


`!4'b010` \longrightarrow `1'b0`

`~4'b010?` \longrightarrow `4'b1101`

width { $\overbrace{0 + (!0?)^{32}}$ } `32'b0`

value { $\begin{matrix} & 1 \\ 0 & 0 \end{matrix}$ }

 Exercise 8: An array declared as `logic [15:0] n;` and has the value `16'h1234`. What are the values and widths of the following expressions?



$$\underline{n[15:13]}_3 \quad \begin{array}{l} 3'b000 \\ 3'd0 \end{array}$$

$$\underline{!n} \quad 1'h0$$

$$\sim n[3:0] \quad \begin{array}{l} 4'b1011 \\ 4'hb \end{array}$$

$$n >> 4 \quad 16'h0123$$

$$n + 1'b1 \quad 16'h1235$$

$$\begin{array}{l} 8'h34 - 4'h4 \\ \underline{(n[7:0]) - (n[3:0])}_8 \end{array} \quad 8'h30$$

$$\underline{n >= 16'h1234}_{1bit} \quad 1'h1$$

$$\begin{array}{l} n \wedge '1 \\ = n \wedge 16'hffff \\ = 16'hedcb \end{array}$$



$$\begin{array}{l} 1'b1 \& 1'b0 \\ n \& \& (!n) \\ \underline{\quad}_1 \end{array} \quad 1'b0$$

$$\underline{n * ((!n) + 1'b1)}_{16} \quad 16'h1234$$

$$\underline{1'b1 + 1'b1}_1 \rightarrow 1'b0 \quad \begin{array}{r} 1 \\ + 1 \\ \hline 0 \end{array}$$

$$\left(\underbrace{1'b1 + 1'b1}_{1} \right) + \underbrace{2'b0}_{2}$$

$$\begin{array}{r} 01 \\ 01 \\ 00 \\ \hline 10 \end{array}$$

$$(1'b1 + 1'b1)$$

$$n = (1'b1 + 1'b1)$$

$$\begin{array}{r} 0001 \\ \hline 0010 \end{array}$$

$$= 1'd35$$

Exercise 9: What are the width and value of the expression: 3 ?

16'd10 : 8'h20?

$$\uparrow \quad 16'h a$$

If x has the value 0, what is the value of the expression: $\overset{0}{x}$?

1'b1 : 1'b0?

$$\uparrow \quad 1'b 0$$


If x has the value -1?

$$1'b1$$

(-1 is non-zero).


Exercise 10: Draw the schematics corresponding to:

$y = a ? (b ? s1 : s2) : (c ? s3 : s4);$

 


evaluate Right to Left.


$y = (a ? s1 : (b ? s2 : (c ? s3 : s4);$

 

$y = (a ? (b ? (c ? s3 : s4) : s2) : s1);$

 

 Exercise 11: Use slicing and concatenation to compute the byte-swapped value of an array `n` declared as `logic [15:0] n`.



$\{ \}$, $[7:0]$

$\{n[7:0], n[15:8]\}$

`logic [15:0] m;`
`assign m = {n[7:0], n[15:8]} ;`

Exercise 12: If `n` has the value `16'h1234`, what are the value and width of:


$\{n[7:0], n[15:8], 4'b1111\}$
 $\underline{\hspace{1cm}}, \underline{\hspace{1cm}}, \underline{\hspace{1cm}}_4$
`20'h 3412f`

Exercise 13: Use concatenation to shift `n` left by two bits.

$\{n[13:0], 2'b00\}$

 Exercise 14: Use concatenation to assign the high-order byte of `n` to `a` and the low-order byte to `b`.

assume `a, b` are declared `a [7:0]`
 $\{a, b, c\} = n$;
 $[7:0] \quad [7:0] \quad [1:0]$ 15:0



`logic x;`
`logic [0:0] x;` $x = 1'b1$
 $x \& 1$
 $x[0]$


Exercise 15:

```
assign y = a + 1 ;
```

Some software warns about truncation. How could you re-write the **assign** statement to avoid such a warning?


$$y = a + 1'b1;$$

 Exercise 16: Write an **always_ff** statement that toggles (inverts) its one-bit output on each rising edge of the clock.



```
always_ff @(posedge clk)
    q <= !q;
```

Exercise 17:

 

Identify the following in the diagram above: component names, component "instance names," component port names, module port names. Label the signal **t** in the schematic.

Exercise 18: Rewrite the **ex60** module using operators. Which version – "structural" or "behavioural" – is easier to understand?

```
module ex60 ( input logic x, y, z,
              output logic c );
```

```
    logic t ;
```

```
    ex1 ex1_1 ( x, y, t ) ;
```

```
    ex1 ex1_2 ( z, t, c ) ;
```

```
endmodule
```

```
→ assign c = x | y | z ;
```

↑
behavioural description
(preferred)