

Examples of State Machines

Exercise 1:

```
module ex83 ( input reset, clk,
              output logic [7:0] y ) ;
```

```
    logic [2:0] n ;
    logic [7:0] seq [0:7] = '{ 3, 5, 1, 7, 6, 1, 8, 9 } ;
```

```
    always_ff @(posedge clk) n
        <= reset ? '0 : n+1 ;
```

```
    assign y = seq[n] ;
```

```
endmodule
```

(a) change these

How would you: (a) change the values in the sequence? (b) change the length of the sequence to 6? (c) stop at the last value?

(b) → count 0 to 5 & repeat:

```
always_ff @(posedge clk) n <=
    reset || n == 5 ? '0 : n+1 ;
```

(c) → stop at n=7

```
always_ff @(posedge clk) n <=
    reset ? '0 :
    n == 7 ? 7 :
    n+1 ;
```

Exercise 2:

```
module ex82 ( output logic unlock,
              input logic [3:0] in,
              input logic clk ) ;
```

```
    logic [2:0] n ;
```

```
    always_ff @(posedge clk) n
```

```
        <= n == 0 && in == 4 ? 1 :
           n == 1 && in == 7 ? 2 :
           n == 2 && in == 2 ? 3 :
           n == 3 && in == 4 ? 4 :
           0 ;
```

```
    assign unlock = n == 4 ;
```


```
endmodule
```

logic [3:0] lut [0:3] = '{ 4, 7, 2, 4 } ;

<= in == lut[n] ? n+1 : 0 ;

Rewrite the module to store the sequence in an unpacked array as in the previous example.

 Exercise 3: Write the body of a Verilog module named **edge** with input **in** and output **out** that implements the rising-edge detector.



```


logic [1:0] d;
always_ff @(posedge clk) d <=
    d == 2'b00 && in == 1 ? 2'b01 :
    d == 2'b01 && in == 1 ? 2'b11 :
    d == 2'b11 && in == 0 ? 2'b00 :
    d == 2'b01 && in == 0 ? 2'b00 :
    d;
assign out = d == 2'b01 ? 1 : 0;

```

Exercise 4: Write the state transition table for this state machine.

state	reset	count	next state
xx	1	xx	00
00	0	0	01
01	0	0	10
10	0	0	11
11	0	0	00

 Exercise 5: Write **always_ff** statements that implement these state machines.



```

always_ff @(posedge clock)
    out <= count != 0 ? out : in;

localparam N = 50_000;

```

count	in == out	next count
x	1	N - 1
0	x	N - 1
n	0	n - 1

```

always_ff @(posedge clock)
    count <= in == out ? N - 1 :
    count == 0 ? N - 1 :
    in != out ? count - 1 :
    count;

```