 


Hierarchical Design

Exercise 1:



Draw a diagram for this instantiation of the `bits` module. Label the module, instance, signal and port names as in the diagram above.

Exercise 2:

```
module sr3bytes
(
    input logic [7:0] newest,
    output logic [7:0] oldest,
    input logic clock
) ;

localparam nbits = 8 ;

logic [nbits-1:0] a, b ;

// matching by order
bits #(nbits) b0 (newest,a,clock);

// matching by name (order does not matter)
bits #(.nb(nbbits)) b1 (.q(b),.clock,.d(a));

// wildcards for names that match
bits #(.nb(nbbits)) b2 (.d(b),.q(oldest),.*);

endmodule
```

Identify the module instantiation statements in the code above. For each one, what is the instantiated module's name? The instance name?

Exercise 3:

```
// traffic light controller

module ex70
( output logic [5:0] lights,
  input logic reset, clk );

  logic [1:0] state ; // state register
  logic [4:0] count ; // delay counter
  logic [5:0] lut [4] = '{ 6'b100_001, 6'b100_010,
                          6'b001_100, 6'b010_100 } ;

  // lights state (counter)
  always @(posedge clk) state
    <= reset ? 2'b00 :
      state == 2'b11 && count == 0 ? 2'b00 :
      count == 0 ? state + 1'b1 :
      state ;

  // set output based on state
  assign lights = lut[state] ;

  // timer
  always @(posedge clk) count
    <= reset ? 29 :
      count != 0 ? count-1 :
      state == 2'b00 || state == 2'b10 ? 4 : 29 ;

endmodule
```

Write a **counter** module with a width parameter *w*, *w*-bit inputs and outputs **d** and **q**, **enable**, **load** and **down** control inputs, and a clock **clk**. The default counter width should be 4 bits, the default value of **enable** should be 1, and the default values of **load**, **down** and **d** should be 0. Rewrite the traffic light controller module by instantiating two instances of this module.