 


Hierarchical Design

Exercise 1:

Draw a diagram for this instantiation of the **bits** module. Label the module, instance, signal and port names as in the diagram above.



Exercise 2:

```
module sr3bytes
(
    input logic [7:0] newest,
    output logic [7:0] oldest,
    input logic clock
);

localparam nbits = 8 ;
logic [nbits-1:0] a, b ;

// matching by order
bits #(nbits) b0 (newest,a,clock);

// matching by name (order does not matter)
bits #(.nb(nbits)) b1 (q(b),.clock,.d(a));

// wildcards for names that match
bits #(.nb(nbits)) b2 (.d(b),.q(oldest),.*);
endmodule
```

module
name
is
bits

instance names

Identify the module instantiation statements in the code above. For each one, what is the instantiated module's name? The instance name?

```
// traffic light controller
```

```
// generic counter module

module counter #( parameter w=4)
  ( output logic [w-1:0] q,
    input logic [w-1:0] d,
    input logic enable, load, down, clk );

  always_ff @(posedge clk)
    q <= ! enable ? q :
         load ? d :
         down ? q-1 : q+1 ;

endmodule
```

```
// traffic light controller

module tlc
( output logic [5:0] lights,
  input logic reset, clk );

  logic [1:0] state ; // state register
  logic [4:0] count ; // delay counter
  logic [5:0] lut [4] = '{ 6'b100_001, 6'b100_010,
                          6'b001_100, 6'b010_100 } ;

  // lights state (counter)
  // always @(posedge clk) state
  //   <= reset ? 2'b00 :
  //   state == 2'b11 && count == 0 ? 2'b00 :
  //   count == 0 ? state + 1'b1 :
  //   state ;

  counter #(w(2)) c_state
    (.q(state), .d(0),
     .enable(reset || count == 0), .load( reset || state == 2'b11 && count == 0 ),
     .down(0),
     .clk );

  // set output based on state
  assign lights = lut[state] ;

  // timer
  // always @(posedge clk) count
  //   <= reset ? 29 :
  //   count != 0 ? count-1 :
  //   state == 2'b00 || state == 2'b10 ? 4 : 29 ;

  counter #(w(5)) c_timer
    (.q(count), .d( reset ? 29 : ( state == 2'b00 || state == 2'b10 ) ? 4 : 29 ),
     .enable(1), .load(reset || count == 0), .down(1),
     .clk );

endmodule
```