 


Analog Interfaces


Exercise 2: What minimum sampling rate would be required to digitize a 10 kHz square wave if you wanted to be able to recover frequency components up to the 7th harmonic (at 70 kHz)?

$$f_{\text{sample}} > 2 \times 70 \text{ kHz} \\ > 140 \text{ kHz}$$



 Exercise 3: A signal with range of $\pm 3 \text{ V}$ must be quantized so that the maximum quantization error is less than 1 mV. What is the resolution in mV? What minimum number of bits of resolution is required?


$$\Delta \leq \frac{V}{2^n} = \frac{6 \text{ V}}{2^n} = 0.002 \text{ V}$$



$$\log_2(2^n) = \log_2\left(\frac{6}{0.002}\right)$$

$$n \geq 11.55$$



use $n = 12$ bits of resolution

 

$\Delta < 2 \text{ mV}$
error $< 1 \text{ mV}$

  Exercise 4: When quantizing a full-scale sine wave, what quantization SNR would be achieved with a resolution of 12 bits? What if the signal's voltage range was only half of the full-scale range?

$$n = 12 \quad \text{SNR (dB)} = 1.76 + 6n = 1.76 + 6 \cdot 12 \\ = 73.76 \quad \frac{S}{N} = 10^{\frac{74}{10}}$$



$$\frac{S}{N} = \frac{1}{2} = 10^{\frac{-6}{10}} \approx -$$

$$P = V^2$$

$$P_1 = V_1^2$$


$$P_2 = V_2^2 = \left(\frac{V_1}{2}\right)^2 = \frac{V_1^2}{4}$$

$$\text{new SNR} = \frac{S/4}{N} \Big|_{\text{linear}} \Leftrightarrow \frac{S}{N} - 6 \text{ dB} \\ = 74 - 6 = 68 \text{ dB}$$

also; now using 11 bits

$$\text{SNR (dB)} = 1.76 + 6 \cdot 11 = 68 \text{ dB}$$

 Exercise 8: You are using a PWM DAC to convert a 200 VDC supply to a 48 VDC output. The clock frequency is 25 kHz. What is the pulse duration?



$$T_{\text{clock}} = \frac{1}{25 \text{ kHz}} = 40 \mu\text{s}$$

$$V_o = V_{\text{ref}} \cdot \frac{t}{T} \quad \frac{t}{T} = \frac{48}{200}$$

$$48 = 200 \cdot \frac{t}{T} \checkmark$$

assume $n = 10$ $2^n = 1024$

$$T = T_{\text{clock}} \cdot 2^n = 40 \mu\text{s} \cdot 1024 \approx 40 \text{ ms}$$

$$t = T \cdot \frac{48}{200} = 40 \times 10^{-3} \cdot \frac{48}{200} =$$



Exercise 9: You are designing a PWM DAC and need resolution of 1 mV with a full-scale output of 12 V. How many bits of resolution are required? The pulse frequency is 10 kHz. What is the clock frequency?

$$\frac{12 \text{ V}}{1 \text{ mV}} = 12,000$$

$$2^n \geq 12,000$$

$$n \geq \log_2 12,000 \geq 13.5$$

Use $n = 14$

  

$$T_{\text{clock}} = \frac{T}{2^n} = \frac{1}{10 \times 10^3 \cdot 2^{14}} =$$

$$T = \frac{1}{10 \times 10^3} \text{ s}$$

Exercise 10: Rank the different DACs described above in terms of sampling rate relative to clock rate and complexity relative to resolution.


binary-weighted : $f_{\text{sample}} = f_{\text{clock}}$

$\Sigma \Delta$: $f_{\text{sample}} \approx \frac{f_{\text{clock}}}{2^n}$

PWM DAC : $f_{\text{sample}} < \frac{f_{\text{clock}}}{2^n}$


fastest
↓
slowest

Exercise 11:

 


Draw a diagram showing the voltage ranges, the comparator outputs and the binary output for the 4-bit flash ADC above.

Exercise 12: How many states will be required for each conversion of an n -bit SAR ADC?

 

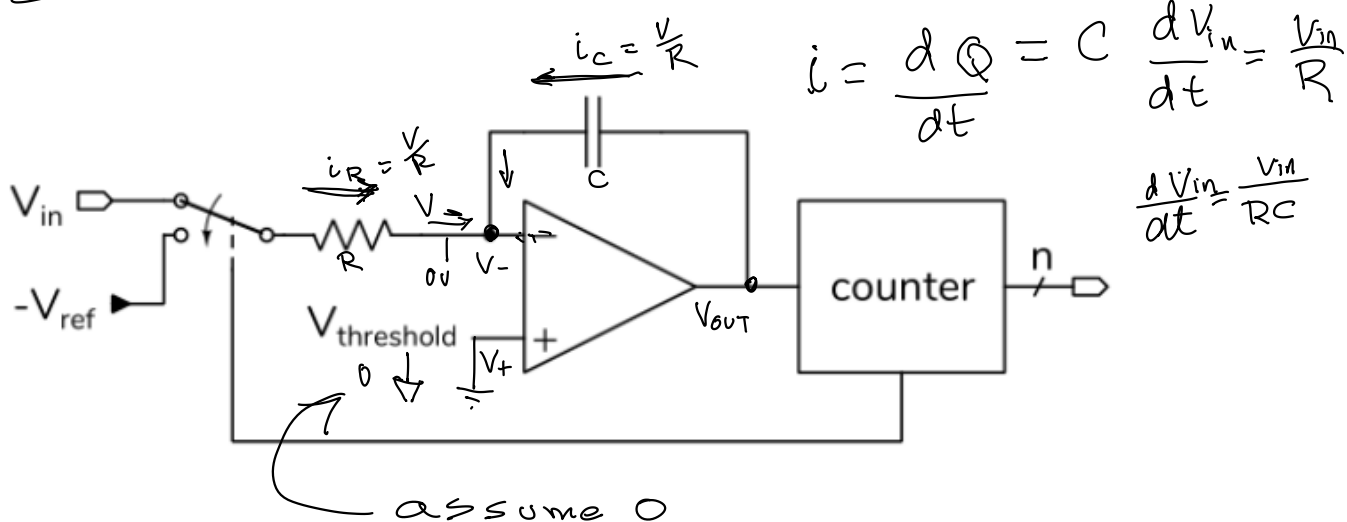Exercise 14: What is the slope of an integrator, in V/s, when charging a 100 nF capacitor with 5 V through a 100 kΩ resistor?



Op-Amps 101

$$V_{out} = A_v(V_+ - V_-) \quad \text{but} \quad A_v \approx \infty \quad \therefore V_+ \approx V_-$$

$$Z_{in} = \infty \quad \therefore i_+ \approx i_- \approx 0$$

$$\text{slope} = \frac{V}{RC} = \frac{5}{100 \times 10^{-9} \times 100 \times 10^3}$$

$$= \frac{5}{10^4 \times 10^{-6}} = \frac{5}{10^{-2}} = \boxed{500 \text{ V/s}}$$