

## Solutions to Midterm 1

There were two versions of each question. The questions and answers for both versions are given below.

### Question 1

Fill the table below with the value of each expression as a Verilog numeric literal including the correct width and the correct value in *hexadecimal* base. Assume the following declarations:

```
logic [3:0] x ;
logic [7:0] y ;
```

and that  $y$  has the value  $8'h83$  (or  $8'h5A$ ) and that  $x$  has the value  $4'b0110$ . The first row has been filled in as an example. You need not show your work or draw another box around the answer.

expression	value
$y[3:0]$	$4'h3$ or $4'hA$
$y[5:0] + x * x$	
$x \&\& ! ( 8 \& y ) ^ 1$	
$\sim y \& 1 ? \sim ( y \& 1 ) ?$ $0 : 1 : 2$	

### Answers

For  $y = 8'h83$ :


expression	value
$y[3:0]$	$4'h3$
$y[5:0] + x * x$	$6'h27$
$x \&\& ! ( 8 \& y ) ^ 1$	$1'h0$
$\sim y \& 1 ? \sim ( y \& 1 ) ?$ $0 : 1 : 2$	$32'h2$

and for  $y = 8'h5a$ :


expression	value
$y[3:0]$	$4'ha$
$y[5:0] + x * x$	$6'h3e$
$x \&\& ! ( 8 \& y ) ^ 1$	$1'h1$
$\sim y \& 1 ? \sim ( y \& 1 ) ?$ $0 : 1 : 2$	$32'h0$
 
### Question 2

Write a Verilog module named `adj` (or `ctrl`) that implements the following block diagram. The diagram follows the course conventions for block diagrams. Follow the course coding guidelines but omit comments.



OR:

 

### Answers

```
module adj
( output logic [11:0] y,
  input logic [9:0] x,
  input logic shift, clock ) ;

always_ff @(posedge clock)
  y <= y >= 50 ? y : shift ? y << 1 : x[9:1] ;
```

```
endmodule
```

```
module ctrl
( output logic [9:0] s,
  input logic [7:0] mx,
  input logic hold, clk ) ;

always_ff @(posedge clk)
  s <= hold ? s : !s ? {mx,2'b11} : s>>1 ;


endmodule
```

### Question 3

**First Version** A state machine with two bits of state and three states controls a motor. The states are:

**00** (stopped), **10** (reversed) and **01** (forward). The output of the state machine is the two bits of state. There are two bits of input: **fwd** (forward) and **rev** (reverse).

 
Write the truth table corresponding to the following state transition diagram:



**Second Version** A state machine with two bits of state and three states controls a motor. The states are: **00** (stopped), **10** (slow) and **11** (fast).

The output of the state machine is the two bits of state. There are two bits of input: **go** (to speed up) and **stop** (to stop).

 Write the truth table corresponding to the following state transition diagram:



Your table must include the state, input and next state. You may, but are not required to, use any of the simplification conventions described in the lecture notes.

## Answers

**First Version** We can list all possible combination of state and input and show the next state:

state	fwd	rev	next state
00	0	0	00
00	0	1	10
00	1	0	01
00	1	1	00
01	0	0	01
01	0	1	00
01	1	0	01
01	1	1	01
10	0	0	10
10	0	1	10
10	1	0	00
10	1	1	10

But using the simplification that there are no state changes if none of the conditions in the table match, this can be written using one row per possible state transition:

state	fwd	rev	next state
00	0	1	10
00	1	0	01
01	0	1	00
10	1	0	00

**Second Version** As in the previous version of the question, the simplified truth table only needs one row per transition arrow in the diagram:

state	fwd	rev	next state
00	1	0	10
10	1	0	11
10	0	1	00
11	0	1	00