

ELEX 2117 : Digital Techniques 2
2025 Winter Term

MIDTERM EXAM 2
2:30 PM –
Wednesday, March 5, 2025
SW01-1205

This exam has four (4) questions on two (2) pages. The marks for each question are as indicated. There are a total of nineteen (19) marks. Answer all questions. Write your answers and all rough work in this paper and nowhere else. Show your work. Underline or draw a box around your final answer. Numerical answers must include units. Books and notes are allowed. No electronic devices other than calculators are allowed. **Show your work.**

This exam paper is for:

Sample Exam 1 A00123456

Each exam is equally difficult.

Answer your own exam.

Do not start until you are told.

Name: _____


BCIT ID: _____

Signature: _____

 Question 1

3 marks

Write a Verilog module named **maxcount** with logic inputs named **reset** and **clock**, an 8-bit logic array input named **max**, a 4-bit logic array input named **inc**, and an 8-bit logic array output named **val**.



The output only changes on the rising edge of **clock**. If **reset** is asserted or **val** is equal to zero then **val** is set to **max**, otherwise **val** is decremented by **inc**. Follow the course coding guidelines but omit comments.

Question 2

6 marks

Write a Verilog testbench module named **maxcount_tb** that:

- declares any necessary variables
- instantiates the module **maxcount** described in the previous question
- sets **max** to a value equal to the last two digits of your BCIT ID and **inc** to 4
- creates a continuous 10 MHz clock, starting with a low (0) value
- asserts reset for exactly one clock cycle
- terminates (rather than pauses) the simulation when **val** is equal to 0

You need not include comments or create a **.vcd** file.

Question 3

4 marks

Given the following module declarations:


```

module rom #(parameter b, w)
( input logic [w-1:0] a,
  output logic [b-1:0] d ) ;

module cpu #(parameter b, w)
( input logic clk, reset,
  input logic [b-1:0] din,
  output logic [b-1:0] dout,
  output logic [w-1:0] a ) ;

```

 Write a Verilog module named **system** that implements the following diagram:



Declare any additional signals required to implement the diagram, using any valid signal names. Use a value of 8 for the parameter **b** and a value of 16 for the parameter **w** in each instantiation. Use explicit port and parameter names (e.g. **.port(signal)**, **.port**, or **#(.parameter(n))**).


Question 4

6 marks

- (a) The following table shows the voltages on inputs A and B for the circuit shown below. H corresponds to a voltage above the gate threshold voltage and L corresponds to 0 V.

Fill in the last column of the table with the voltage at point F of the circuit. Use H for a voltage of approximately V_{dd} and L for a voltage of approximately 0 V.

A	B	F
L	L	
L	H	
H	L	
H	H	

 

- (b) An IC has specifications of $V_{IL} = 0.3 \text{ V}$ and $V_{IH} = 0.7 \text{ V}$. If you needed a noise margin of 0.2 V for both high and low voltages, what are the required maximum V_{OL} and minimum V_{OH} ?
- (c) A circuit draws 200 mA when operating with a clock frequency of 50 MHz. You would like to operate this circuit for a year when powered by a CR2016 battery that has a capacity of 100 mAh. What clock frequency should you use? *Hints: $P = IV$. V does not change. There are $365 \times 24 = 8760$ hours in a year.*

ELEX 2117 : Digital Techniques 2

2025 Winter Term

MIDTERM EXAM 2

2:30 PM –

Wednesday, March 5, 2025

SW01-1205

This exam has four (4) questions on two (2) pages. The marks for each question are as indicated. There are a total of nineteen (19) marks. Answer all questions. Write your answers and all rough work in this paper and nowhere else. Show your work. Underline or draw a box around your final answer. Numerical answers must include units. Books and notes are allowed. No electronic devices other than calculators are allowed. **Show your work.**

This exam paper is for:

Sample Exam 2 A01234567

Each exam is equally difficult.

Answer your own exam.

Do not start until you are told.

Name: _____


BCIT ID: _____

Signature: _____

 Question 1

3 marks

Write a Verilog module named **maxcount** with logic inputs named **reset** and **clock**, an 8-bit logic array input named **max**, a 4-bit logic array input named **inc**, and an 8-bit logic array output named **val**.



The output only changes on the rising edge of **clock**. If **reset** is asserted or **val** is equal to **max** then then **val** is set to zero, otherwise **val** is incremented by **inc**. Follow the course coding guidelines but omit comments.

Question 2

6 marks

Write a Verilog testbench module named **maxcount_tb** that:

- declares any necessary variables
- instantiates the module **maxcount** described in the previous question
- sets **max** to a value equal to the last two digits of your BCIT ID and **inc** to 2
- creates a continuous 50 MHz clock, starting with a low (0) value
- asserts reset for exactly one clock cycle
- terminates (rather than pauses) the simulation when **val** is equal to **max**

You need not include comments or create a **.vcd** file.

Question 3

4 marks

Given the following module declarations:

```

module rom #(parameter b, w)
( input logic [w-1:0] a,
  output logic [b-1:0] d ) ;


```

```

module cpu #(parameter b, w)
( input logic clk, reset,
  input logic [b-1:0] din,
  output logic [b-1:0] dout,
  output logic [w-1:0] a ) ;

```

 Write a Verilog module named **system** that implements the following diagram:



Declare any additional signals required to implement the diagram, using any valid signal names. Use a value of 8 for the parameter **b** and a value of 16 for the parameter **w** in each instantiation. Use explicit port and parameter names (e.g. **.port(signal)**, **.port**, or **#(.parameter(n))**).


Question 4

6 marks

- (a) The following table shows the voltages on inputs A and B for the circuit shown below. H corresponds to a voltage above the gate threshold voltage and L corresponds to 0 V.

Fill in the last column of the table with the voltage at point F of the circuit. Use H for a voltage of approximately V_{dd} and L for a voltage of approximately 0 V.

A	B	F
L	L	
L	H	
H	L	
H	H	

 

- (b) An IC has specifications of $V_{IL} = 0.3 \text{ V}$ and $V_{IH} = 0.7 \text{ V}$. If you needed a noise margin of 0.2 V for both high and low voltages, what are the required maximum V_{OL} and minimum V_{OH} ?
- (c) A circuit draws 50 mA when operating with a clock frequency of 50 MHz. You would like to operate this circuit for a year when powered by a CR2016 battery that has a capacity of 100 mAh. What clock frequency should you use? *Hints: $P = IV$. V does not change. There are $365 \times 24 = 8760$ hours in a year.*