

ELEX 2117 : Digital Techniques 2  
2025 Winter Term

Quiz 2

9:30 AM – 10:20 AM

Thursday, January 20, 2024

SW09-110

This exam has two (2) questions on one (1) pages. The marks for each question are as indicated. There are a total of eight (8) marks. Answer all questions. Write your answers and all rough work in this paper and nowhere else. Show your work. Underline or draw a box around your final answer. Numerical answers must include units. Books and notes are allowed. No electronic devices other than calculators are allowed. **Show your work.**

This exam paper is for:

Paper, Test 1 A00123456

Each exam is equally difficult.

Answer your own exam.

Do not start until you are told.

Name: \_\_\_\_\_

BCIT ID: \_\_\_\_\_

Signature: \_\_\_\_\_

## Question 1


4 marks

Given the following module declarations:

```
module bgen #(parameter b)
  ( input logic reset, clk, next,
    output logic [b-1:0] val );

module expand #(parameter b)
  ( input logic reset, clk,
    input logic [b-1:0] t,
    output logic en,
    output logic out );
```

 Write a Verilog module named **tgen** that implements the following diagram:




Declare any additional signals required to implement the diagram, using any valid signal names. Use a value of 4 for the parameter **b** in each instantiation. You may use any of the conventions for associating signals and ports.

## Question 2

4 marks

Write a module named **detect** with one-bit inputs named **clk**, **reset**, and **in**, and a one-bit output named **out**.

 **out** should be set to 1 when the sequence 1, 0, 0, 1 has appeared on **in** on consecutive rising edges of **clk**. When **reset** is asserted it should be assumed all previous and current values of **in** were/are 0. **out** should be set to 1 at the rising edge of **clk** on the last value of the sequence and stay high for one **clk** period. For example:



Any correct solution is acceptable. The timing diagram above shows two possible state variables that you could use. **n** counts the correct number of values seen; **sr** stores the most recent four input values.

ELEX 2117 : Digital Techniques 2

2025 Winter Term

Quiz 2

9:30 AM – 10:20 AM

Thursday, January 20, 2024

SW09-110

This exam has two (2) questions on one (1) pages. The marks for each question are as indicated. There are a total of eight (8) marks. Answer all questions. Write your answers and all rough work in this paper and nowhere else. Show your work. Underline or draw a box around your final answer. Numerical answers must include units. Books and notes are allowed. No electronic devices other than calculators are allowed. **Show your work.**

This exam paper is for:

Paper, Test 2 A00123456

Each exam is equally difficult.

Answer your own exam.

Do not start until you are told.

Name: \_\_\_\_\_

BCIT ID: \_\_\_\_\_

Signature: \_\_\_\_\_

## Question 1


4 marks

Given the following module declarations:

```
module bgen #(parameter b)
  ( input logic reset, clk, next,
    output logic [b-1:0] val );
```

```
module expand #(parameter b)
  ( input logic reset, clk,
    input logic [b-1:0] t,
    output logic en,
    output logic out );
```

 Write a Verilog module named **tgen** that implements the following diagram:




Declare any additional signals required to implement the diagram, using any valid signal names. Use a value of 4 for the parameter **b** in each instantiation. You may use any of the conventions for associating signals and ports.

## Question 2

4 marks

Write a module named **detect** with one-bit inputs named **clk**, **reset**, and **in**, and a one-bit output named **out**.

 **out** should be set to 1 when the sequence 0, 1, 1, 0 has appeared on **in** on consecutive rising edges of **clk**. When **reset** is asserted it should be assumed all previous and current values of **in** were/are 1. **out** should be set to 1 at the rising edge of **clk** on the last value of the sequence and stay high for one **clk** period. For example:



Any correct solution is acceptable. The timing diagram above shows two possible state variables that you could use. **n** counts the correct number of values seen; **sr** stores the most recent four input values.