

Solutions to Quiz 2

There was one version of Question 1 and two versions of Question 2. The values and the answers for all versions are given below.


Question 1

Given the following module declarations:

```
module bgen #(parameter b)
  ( input logic reset, clk, next,
    output logic [b-1:0] val );

module expand #(parameter b)
  ( input logic reset, clk,
    input logic [b-1:0] t,
    output logic en,
    output logic out );
```

 Write a Verilog module named **tgen** that implements the following diagram:



Declare any additional signals required to implement the diagram, using any valid signal names. Use a value of 4 for the parameter **b** in each instantiation. You may use any of the conventions for associating signals and ports.

Answers

The following code generates the block diagram shown in the quiz. The **tgen** module shows different ways the **bgen** and **expand** modules could be instantiated.

```
// ELEX 2117 202510 Quiz 2 Question 1 - Example
// Ed.Casas 2025-2-22

// output next value in table 'tab' when 'next' asserted

module bgen #(parameter b)
  ( input logic reset, clk, next,
    output logic [b-1:0] val );

  logic [b-1:0] tab [7] = '{ 3, 1, 1, 3, 2, 2, 3 };
  logic [3:0] i ;

  always_ff @(posedge clk) i
    <= reset ? '0 : next ? ( i == $size(tab)-1 ? '0 :
      i + 1'b1 ) : i ;
```

```
  assign val = tab[i] ;

endmodule

// set 'out' alternating low/high for duration 't'
// asserts 'en' to get next duration

module expand #(parameter b)
  ( input logic reset, clk,
    input logic [b-1:0] t,
    output logic en, out );

  logic [b-1:0] i ;

  // count down the duration of each pulse
  always_ff @(posedge clk) i
    <= reset ? '0 : i == 0 ? t-1'b1 : i - 1'b1 ;

  // alternate +ve and -ve pulses
  always_ff @(posedge clk) out
    <= reset ? '0 : en ? !out : out ;

  // get next duration when start one
  assign en = i == 0 ;

endmodule

// example test waveform generator
// instantiates 'bgen' and 'expand'

module tgen
  ( input logic reset, clk,
    output logic wave );

  localparam b = 4 ;

  logic en ;
  logic [b-1:0] t ;

  // equivalent instantiations:

  // bgen #(4) b0 ( reset, clk, e, t ) ;
  // bgen #(.b(4)) b0 ( .reset(reset), .clk(clk),
  //   .next(en), .val(t) ) ;
  // bgen #(.b(4)) b0 ( .reset, .clk,
  //   .next(en), .val(t) ) ;
  bgen #(.b(4)) b0 ( .next(en), .val(t), .* ) ;

  // expand #(4) e0 ( reset, clk, t, e, wave ) ;
  // expand #(.b(4)) e0 ( .reset(reset), .clk(clk),
  //   .t(t), .en(en), .out(wave) ) ;
  // expand #(.b(4)) e0 ( .reset, .clk,
  //   .t, .en, .out(wave) ) ;
  expand #(.b(4)) e0 ( .out(wave), .* ) ;

endmodule

module tgen_tb ;
  logic reset, clk ;
```

The (post-reset portion of) the **wave** output from **tgen** shown below is also the **in** waveform used in the next question.



Write a module named **detect** with one-bit inputs named **clk**, **reset**, and **in**, and a one-bit output named **out**.

The timing diagram illustrates the sequence of signals for a reset operation. The signals are defined as follows:

- reset=1**: A pulse that occurs at the start of the sequence.
- pin=1**: A signal that is high during the first two clock cycles.
- clk=0**: A clock signal that is high for the first two clock cycles and then alternates between high and low for the remaining 14 cycles.
- out=x**: A signal that is high for the first two clock cycles and then alternates between high and low for the remaining 14 cycles.
- n(2)=x**: A signal that is high for the first two clock cycles and then alternates between high and low for the remaining 14 cycles.
- st(2)=xxxx**: A signal that is high for the first two clock cycles and then alternates between high and low for the remaining 14 cycles.

The diagram shows the following sequence of events:

- Reset is asserted (reset=1) at the start of the sequence.
- The pin signal (pin=1) is high for the first two clock cycles.
- The clock signal (clk=0) is high for the first two clock cycles and then alternates between high and low for the remaining 14 cycles.
- The output signal (out=x) is high for the first two clock cycles and then alternates between high and low for the remaining 14 cycles.
- The status signal (n(2)=x) is high for the first two clock cycles and then alternates between high and low for the remaining 14 cycles.
- The status signal (st(2)=xxxx) is high for the first two clock cycles and then alternates between high and low for the remaining 14 cycles.

Timing diagram showing the relationship between reset, cs, oe, r2d0-ex, and spi3d0-mux signals over time. The diagram includes a clock signal and data bus signals. The reset signal is active-low. The cs signal is active-low and enables the SPI interface. The oe signal is active-low and enables the output. The output (r2d0-ex) is shown as a bus of 8 bits. The SPI data (spi3d0-mux) is shown as a bus of 8 bits. The diagram illustrates the sequence of events: reset, then cs, then oe, and finally the data transfer.

Answers

There were two versions of this question. The two answers are named **detect_hi** and **detect_low**. Each solution shows two possible design approaches, one using a counter and one using a shift register, although only *one* of these was required.

```

module detect_tb ;

    logic clk, reset ;
    logic in ;
    logic outhi, outlo ;

    detect_hi dh0 (.out(outhi), .*) ;
    detect_lo dl0 (.out(outlo), .*) ;

    int t[] = { 3, 1, 1, 3, 2, 2, 3, 0 } ;

    initial begin
        $dumpfile("detect_tb.vcd") ;
        $dumpvars ;

        { reset, clk, in } = 3'b101 ;
        #1us reset = '0 ;

        for ( int i=0 ; t[i] ; i++ )
            #t[i] in = ~in ;


        #1us $finish ;
    end

    always #0.5us clk = ~clk ;


endmodule
// synthesis translate on

```

 
Running the testbench generates the waveforms shown above and the **detect_lo** version synthesizes to a single state machine:



with a state transition diagram of:

 

 while the **detect_hi** version synthesizes to:



(for some reason the state machine code is also generated).