

Assignment 2

Due Tuesday, May 17. Show your work. Submit your assignment using the appropriate dropbox on the course web site. Assignments submitted after the solutions are made available will be given a mark of zero.

Note: Answers to any of the following questions must follow the course restrictions on writing VHDL. In particular, the restrictions on process statements and registering outputs (if applicable). Use `std_logic[_vector]` and unsigned types.

Question 1

Draw a schematic diagram for the following VHDL code. Label signals with the names used in the VHDL code. Use conventional schematic symbols for multiplexers, flip-flops and boolean operators. Use labelled blocks for VHDL arithmetic or comparison operators. Draw conditional assignments using multiple **two-input** multiplexers. Label each multiplexer input with the corresponding value of the select input. Show the bus widths on multi-bit signals.

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
...
architecture rtl of asg2q4 is
    signal a, b : unsigned (2 downto 0) ;
    signal c, d : unsigned (7 downto 0) ;
    signal x, y, z : std_logic ;
begin

    with a select b <=
        "000" when "111",
        "111" when "000",
        "010" when others ;

    process(x)
    begin
        if x'event and x='1' then
            a <= b ;
            c <= d ;
        end if ;
    end process ;

    d <=
        to_unsigned(127,d'length) when y = '1' and z = '1' else
        to_unsigned( 0,d'length) when y /= z else
        to_unsigned(255,d'length) when c > 2 else
        to_unsigned( 1,d'length) ;


    y <= '1' when a < 5 else '0' ;

end rtl ;

```

 Question 2

Write a VHDL entity and architecture for the following schematic:




don't worry about whether the circuit does something useful (it doesn't) – just write the VHDL that would implement it. The numbers in brackets are ranges of subscripts (e.g. `x[2:0]` is `x(2 downto 0)`).

The inputs and outputs are denoted by the connector symbols (i.e. outputs are `h` and `m` and the input is `clock`).

 Question 3

Write a VHDL entity and architecture for the following schematic:



All multiplexers are 12 bits wide.

Question 4

Write the VHDL entity and architecture for a controller that will “slow start” a motor. Your controller has two one-bit outputs: `on` and `fast` and three one-bit inputs `start`, `stop` and `speed`.

When the `start` input is high the `on` output should be set high until the `speed` input is high and then both `on` and `fast` should be set high. If at any time the `stop` input is high then both `on` and `fast` should be set to off. If `start` and `stop` are both low or both high then there should be no change in the outputs.

Question 5


Write a VHDL entity and architecture for a circuit that has a 1 MHz clock input called `clk`, an active-low synchronous reset input `reset_n`, and an output called `pulse2` that is high for $2\ \mu\text{s}$ once every $20\ \mu\text{s}$.

Question 6

Write the VHDL architecture for the entity:

```
entity controller is
  port ( en, f, clk : in std_logic ;
        G, Y : out std_logic ) ;
end controller ;
```

 that implements a state machine with the following state transition diagram:



where the output `G` is 1 in states `A` and `B` and 0 otherwise and the output `Y` is 1 in state `B` and 0 otherwise. The transition condition `a` is that `en` is 1. The transition condition `b` is that `f` and `en` are both 1. The state remains the same for all other input conditions. State transitions happen on the rising edge of `clk`.