


```

signal state, next_state : std_logic_vector (1 downto 0) ;
begin

on_out <= state(0) ;
fast  <= state(1) ;

next_state <=
"01" when state = "00" and start = '1' else
"11" when state = "01" and speed = '1' else
"00" when stop = '1' and start = '0' else
state ;

process (clock)
begin
if clock'event and clock = '1' then
state <= next_state ;
end if;
end process;

end rtl;

```

A missing clock input was added and the name of the on output was changed to on_out because on is a reserved word in VHDL. To make the code more compact (at the cost of some readability) I used a 2-bit state variable instead of an enumerated type.

Question 5

Here is a simple solution for a resettable clock divider that outputs a 2-period-long output once every 20 clock periods:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity sol2q5 is
port (
clk, reset_n : in std_logic;
pulse2      : out std_logic);
end sol2q5;

architecture rtl of sol2q5 is
signal count, next_count : unsigned (4 downto 0);
signal next_pulse2 : std_logic;
begin

next_count <=
to_unsigned(0,count'length) when reset_n = '0' or count = 19 else
count + 1 ;


next_pulse2 <=
'1' when count = 18 or count = 19 else
'0' ;

process (clk)
begin
if clk'event and clk = '1' then
count <= next_count ;
pulse2 <= next_pulse2 ;
end if;
end process;

end rtl;

```

 Note that we register the output so that it is glitch-free. It is now delayed by one clock period relative to the value of count. The simulation results are:



Many other solutions are possible:

- since it's often simpler for hardware to check for a value of 0 (and 1) the implementation might be simpler if we counted down from 19 instead of counting up from 0,
- we might (or might not) get a simpler implementation by using a divide-by-2 stage followed by a divide-by-10 (or even divide by-2, -2 and -5) – all synchronous, of course,
- a 5-bit [linear-feedback shift-register](#) would replace the adder with an xor gate,
- a [one-hot encoding](#) with twenty flip-flops might be the fastest implementation on an FPGA (although probably requiring more hardware).
- at very high speeds (but not in this course) we might use a ripple counter.

Question 6

In the following solution I used an enumerated type instead of std_logic_vector values for the state. The outputs are:

State	G	Y
A	1	0
B	1	1
C	0	0

The VHDL code is as follows:

```

library ieee;
use ieee.std_logic_1164.all;

entity controller is
port ( en, f, clk : in std_logic ;
G, Y : out std_logic ) ;
end controller ;

architecture rt of controller is

type states is (A, B, C) ;
signal state, next_state : states ;
signal next_G, next_Y : std_logic;

begin

next_state <=
A when state = B and f = '1' and en = '1' else
A when state = C and en = '1' else
B when state = A and en = '1' else
C when state = B and en = '1' else
state ;

next_G <= '1' when next_state = A or next_state = B else '0' ;
next_Y <= '1' when next_state = B else '0' ;

process (clk)
begin
if clk'event and clk = '1' then
state <= next_state ;
G <= next_G ;
Y <= next_Y ;
end if;
end process;

end rt;

```