

Do not open this exam until you are told.

This exam is for:

Exam Version 3 A00123456

- *This exam has three (3) questions on six (6) pages. Answer all questions.*
- *The marks for each question are as indicated. There are a total of 24 marks.*
- *Write your answers and all rough work in this exam paper **and nowhere else**. Make a note if you continue your answer on the back of a sheet.*
- *Books and notes are allowed. No electronic devices other than calculators are allowed.*
- **You may not leave the exam area until after 4:30 PM. You may not use any electronic equipment other than a calculator until after leaving the exam area. Violation of this instruction will result in a failing mark for the course.**

Name: _____


BCIT ID: _____

Signature: _____

Question	Mark
1	/10
2	/8
3	/6
Total	/24

 Question 1 (10 marks)

This question asks you to design a controller that automatically opens a parachute.



The controller has two active-high altitude-detection inputs `barhi` and `barlo`, an active-low safety switch `safe_n` and a clock input. `barhi` is asserted at 500 m altitude or less. `barlo` is asserted at 100 m or less. `safe_n` is de-asserted when the parachute leaves the plane. `clock` is a one-pulse-per-second clock.


The controller has two active-high outputs: `drogue` and `main`. Both outputs should be set low whenever `safe_n` is asserted. Otherwise `drogue` should be asserted when `barhi` or `barlo` are asserted. `main` should be asserted 5 seconds after `drogue` is asserted or if `barlo` is asserted.

- (a) Write the VHDL entity declaration for the controller called `controller`.
- (b) Write a VHDL architecture that implements the controller.

Use `std_logic` and `unsigned` types only. You do not need to include library and use statements. You do not need to register the outputs.

 Question 2 (8 marks)

Write a VHDL entity and architecture corresponding to the following schematic:



Use `std_logic` for single-bit signals (those where the bus width is not shown) and `unsigned` for multi-bit signals. Blocks labelled +/-1 add/subtract one from their inputs. Signals labelled in the schematic are entity inputs or outputs. You may choose any name(s) for signals within the architecture.

Question 3 (6 marks)

Draw the schematic corresponding to the following VHDL code:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

architecture behav of exam is
    signal wave, waven : unsigned (14 downto 0) ;
    signal set, up, tick : std_logic ;
begin

    waven <=
        to_unsigned(1234,15) when set = '1' else
        wave+2 when up = '1' else
        wave ;

    process(tick)
    begin
        if tick'event and tick = '1' then
            wave <= waven ;
        end if ;
    end process ;

end behav;
```

Label all signals with their names. Use conventional schematic symbols. Draw conditional assignments using multiple **two-input** multiplexers. Label each multiplexer input with the corresponding value of the select input. Show the bus widths for multi-bit signals.