 


Solutions to Final Exam

Question 1

There were three versions of this question. Each design was a synchronous counter with reset. The values of the two outputs are determined by the counter and input values. For versions 1 and 2 the reset is `reset` and the clock is `oneml` or `tick`. For version 3 the timer is reset when the drogue output is not asserted and the clock is `clock`. Sample entities and architectures for the three versions are given below.

For version 1 the counter is 9 bits wide and the `slow` and `done` outputs are set high whenever the count is more than 400 and 502 respectively (since the counter is reset for the first two ml):



```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity controller1 is
    port (
        reset, oneml : in std_logic;
        slow, done   : out std_logic);
end controller1;


architecture rtl of controller1 is
    signal level, next_level : unsigned (8 downto 0);
begin
    next_level <=
        to_unsigned(0,level'length) when reset = '1' else
        level + 1 ;

    process (oneml)
    begin
        if oneml'event and oneml = '1' then
            level <= next_level ;
        end if;
    end process;

    slow <= '1' when level >= 400 else '0' ;
    done <= '1' when level >= 500 else '0' ;
end rtl;

```

 For version 2 the counter is 8 bits wide and the `light` and `full` outputs are set high whenever the count is more than 200 and 250 respectively (since the counter is reset for the first two meters):



```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity controller2 is
    port (
        reset, tick : in std_logic;
        light, full : out std_logic);
end controller2;


architecture rtl of controller2 is
    signal dist, next_dist : unsigned (7 downto 0);
begin
    next_dist <=
        to_unsigned(0,dist'length) when reset = '1' else
        dist + 1 ;

    process (tick)
    begin
        if tick'event and tick = '1' then
            dist <= next_dist ;
        end if;
    end process;

    light <= '1' when dist >= 200 else '0' ;
    full <= '1' when dist >= 250 else '0' ;
end rtl;

```

 For version 3 the counter is 3 bits wide. The drogue output is asserted when `safe_n` is high and either `barhi` or `barlo` are high. `main` is asserted if drogue is asserted or the count is more than 5. An internal version of the drogue output is used to avoid reading an output signal.



```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity controller3 is

    port (
        barhi, barlo, safe_n, clock : in  std_logic;
        drogue, main : out std_logic);
end controller3;

architecture rtl of controller3 is

    signal delay, next_delay : unsigned (2 downto 0);
    signal drogue_i : std_logic;

begin

    drogue_i <= safe_n and ( barhi or barlo ) ;

    next_delay <=
        to_unsigned(0,delay'length) when drogue_i = '0' else
        delay + 1 ;

    process (clock)
    begin
        if clock'event and clock = '1' then
            delay <= next_delay ;
        end if;
    end process;

    main <=
        '1' when safe_n = '1' and
            ( drogue_i = '1' or ( delay > 5 ) ) else
        '0' ;

    drogue <= drogue_i ;

end rtl;

```

is:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity question2a is

    port (
        down, set, clk : in  std_logic;
        cnt_out : out unsigned (15 downto 0) );
end question2a ;

architecture rtl of question2a is

    signal cnt, next_cnt : unsigned (15 downto 0);

begin

    next_cnt <=
        x"8000" when set = '1' else
        cnt - 1 when down = '1' else
        cnt ;


    process (clk)
    begin
        if clk'event and clk = '1' then
            cnt <= next_cnt ;
        end if;
    end process;

    cnt_out <= cnt ;

end rtl;

```

The VHDL code corresponding to:

 

is:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity question2b is

    port (
        down, reset, clk : in  std_logic;
        cnt_out : out unsigned (15 downto 0) );
end question2b ;

architecture rtl of question2b is

    signal cnt, next_cnt : unsigned (15 downto 0);


begin


```

Question 2

The three solutions are very similar. Each schematic consists of a synchronous counter that is set/reset/incremented by two control signals.

The VHDL code corresponding to:

 

```


next_cnt <=
  x"0000" when reset = '1' else
  cnt + 1 when down = '1' else
  cnt ;

process (clk)
begin
  if clk'event and clk = '1' then
    cnt <= next_cnt ;
  end if;
end process;

cnt_out <= cnt ;
end rtl;

```

The VHDL code corresponding to:

 

is:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity question2c is
  port (
    up, down, clk : in std_logic;
    count : out unsigned (7 downto 0) );
end question2c ;

architecture rtl of question2c is
  signal cnt, next_cnt : unsigned (7 downto 0);

begin
  next_cnt <=
    cnt - 1 when down = '1' else
    cnt + 1 when up = '1' else
    cnt ;

  process (clk)
  begin
    if clk'event and clk = '1' then
      cnt <= next_cnt ;
    end if;
  end process;

  count <= cnt ;
end rtl;

```

Question 3

A schematic for the following VHDL code:

```


library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

architecture rtl1 of exam is
  signal sig, sig_next : unsigned (7 downto 0) ;
  signal rst, add, clk : std_logic ;
begin
  sig_next <=
    x"00" when rst = '1' else
    sig+1 when add = '1' else
    sig ;

  process(clk)
  begin
    if clk'event and clk = '1' then
      sig <= sig_next ;
    end if ;
  end process ;
end rtl1 ;

```

might be:

 

A schematic for the following VHDL code:

```


library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

architecture rtl2 of exam is
  signal sig, sig_next : unsigned (7 downto 0) ;
  signal rst_n, sub, clk : std_logic ;
begin
  sig_next <=
    x"FF" when rst_n = '0' else
    sig-1 when sub = '1' else
    sig ;

  process(clk)
  begin
    if clk'event and clk = '1' then
      sig <= sig_next ;
    end if ;
  end process ;
end rtl2 ;

```

might be:

 

A schematic for the following VHDL code:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

architecture behavior of exam is
    signal wave, waven : unsigned (14 downto 0) ;
    signal set, up, tick : std_logic ;
begin

    waven <=
        to_unsigned(1234,15) when set = '1' else
        wave+2 when up = '1' else
        wave ;

    process(tick)
    begin
        if tick'event and tick = '1' then
            wave <= waven ;
        end if ;
    end process ;

end behavior;

```

might be:

