


## Solutions to Quiz 4

### Question 1

A communication system uses voltage levels of +5 and 0 volts to transmit data. Voltages between 2 and 3 volts are considered unreliable and equivalent to an error. What is the noise margin of this system?
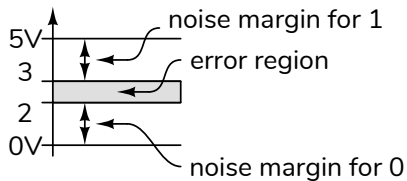
#### Answer

The noise margin is the noise level (voltage in this case) required to cause an error. If +5 is transmitted and a voltage is 3 volts or less is considered an error, then the noise margin is 2 V. Similarly if 0 V is transmitted and 2 V or more is considered an error then the noise margin is 2 V. This is shown below:



### Question 2

A communication system uses differential signalling. You measure the voltages on each of the differential signals relative to ground.

On one signal the voltage switches between 1 volt (for 0) and 3 volts (for 1). On the other signal the voltage switches between 3 volts (for 0) and 1 volts (for 1).

- (a) What is the common-mode voltage?
- (a) What is the differential voltage?

#### Answer

For a 0 the differential voltage is  $(1 - 3) = -2$  V and the common-mode voltage is  $(1 + 3)/2 = 2$  V.

For a 1 the differential voltage is  $3 - 1 = 2$  V and the common-mode voltage is  $(3 + 1)/2 = 2$  V.

### Question 3

A 10 k $\Omega$  pull-up resistor is used at one end of a 10 m transmission line that has a capacitance of 30 pF per meter.

What is the instantaneous slew rate when the voltage across the transmission line begins to be pulled up from 0 V to 10 V?

Hints:

- At the instant that the voltage on the line is 0V the voltage across the resistor is 10V.
- The current into a capacitor is equal to  $CdV/dt$  where  $dV/dt$  is the instantaneous rate of change of the voltage.

#### Answer

When the low-to-high transition begins the voltage across the pull-up resistor is 10 V so the current is  $i = 10 \text{ V}/10 \text{ k}\Omega = 1 \text{ mA} = CdV/dt$ . Solving for the slew rate,  $dV/dt = i/C = 1 \times 10^{-3}/10 \times 30 \times 10^{-12} \approx 3.3 \text{ V}/\mu\text{s}$ .