

## Differential Signalling

**Exercise 1:** What are the differential and common-mode voltages for this example?