


# Baseband Interfaces - Electrical

This lecture covers the electrical aspects of the physical layer of baseband communication systems.
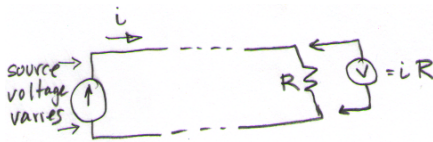
## Current Loops

Data can be transmitted by using different currents rather than different voltages.


Current signalling uses a current source at the transmitter instead of a voltage source. The current swing stays constant regardless of the resistance of the line. The voltage across the terminating resistor at the receiving end always has the same voltage swing regardless of the length of the cable. The current loop's noise margin is thus independent of the length (resistance) of the circuit.



The use of current loops also makes it possible for the transmitter to determine when the loop has failed because it becomes an open circuit and the current stops.
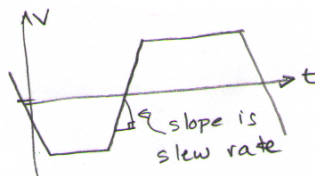
## Slew Rate

Slew rate is the rate (in volts/microsecond) at which a voltage changes as it switches between levels. Limiting the slew rate makes transitions between voltage levels more gradual. This limits the achievable data rate but also limits peak current consumption of the interface ICs and reduces the high-frequency components that are more likely to radiate from transmission lines and cause interference to other devices. Ideally the slew rate would be matched to the data rate so that the transition between voltage levels is a small fraction of the symbol duration.



**Exercise 1:** The RS-232 standard specifies a maximum slew rate of  $30\text{V}/\mu\text{s}$ . Assuming a voltage swing of 30 volts, what is the maximum data rate for which two signal level transitions occupy 10 % of the bit period?

## Impedance Matching


The source (transmitter) and load (receiver) impedances should be the complex conjugate of the transmission line characteristic impedance to avoid reflections. Typically the characteristic impedance is resistive.

## Bus Terminations

Bus Terminations are used at the ends of transmission lines to prevent reflections that would cause inter-symbol interference.

Passive terminations are resistors of a resistance equal to the characteristic impedance of the transmission line.


Active terminations connect the terminating resistor to a low-impedance voltage source with a voltage half-way between the maximum and minimum signalling voltages (e.g 2.5V for a bus that swings between 0 and 5V). This reduces power consumption by a factor of 4 compared to a passive termination.

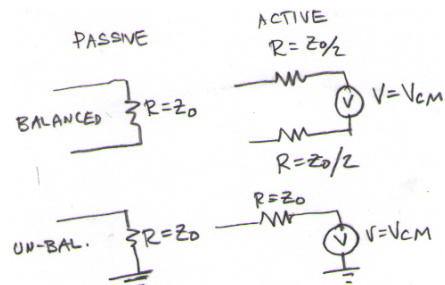

**Exercise 2:** What is the active termination supply voltage for bipolar signalling?
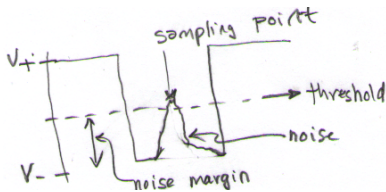
## Noise Margin


Noise margin is the noise level required to cause an error. For example, a bipolar signal received with levels of  $\pm 1V$  would have a noise margin of  $1V$  because a noise voltage of  $1V$  (in the wrong direction) would cause an error.




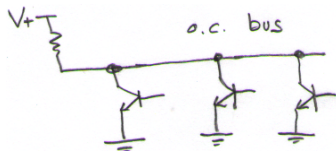
## Tri-State and Open-Collector Outputs

Bus-type network topologies consist of multiple devices connected in parallel to the same transmission line. There are two ways that bus drivers avoid having two outputs connected together.

The first method is to use open-collector (or open drain) outputs. The open-collector outputs can pull the line low but cannot source current or voltage. An external pull-up resistor sets the bus voltage high when none of the open-collector outputs are active. Open-collector outputs are simple to implement and provide all devices an indication that the bus is connected and active. However, the pull-up resistor results in constant power consumption and the RC time constant limits data rates.



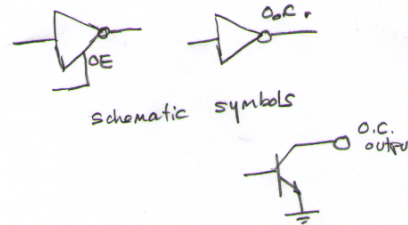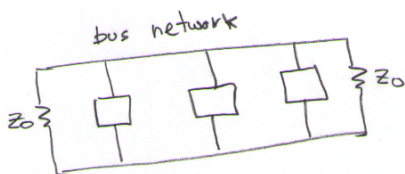The second method is to use bus drivers with tri-state outputs. In addition to high- and low-voltage outputs, tri-state outputs also have a high-impedance output state that effectively disconnects the output from the bus. The design of a bus with tri-state drivers is more complex because some mechanism must be provided to switch each driver on and off at the appropriate times.



## Line Drivers and Receivers

Line drivers and receivers are ICs that interface digital logic circuits to transmission lines. The primary functions of these ICs are:


- convert to/from the voltage or current levels on the transmission line to logic-level signals (TTL, CMOS, etc).
- match the impedance of the transmission line to minimize reflections and maximize power transfer
- limit slew rate to limit interference to other devices
- provide protection from accidental short-circuits and overvoltage or overcurrent conditions
- provide switchable tri-state outputs or open-collector outputs if used on bus-type connections
- detect invalid voltage/current levels or disconnected lines when possible
- detect disconnected or floating transmission lines
- convert unbalanced logic level signals to/from balanced transmission lines (if appropriate)

We will study a typical line driver and receiver in the lab.

## Transformers

Transformers are widely used in baseband communications systems for various reasons.

Transformers can convert between balanced and unbalanced circuits. In this configuration the transformer is called a “balun”. If the balanced side of the transformer has a center-tap then this tap will be at the common-mode voltage. The common-mode circuit can be grounded, used to carry power (as in “power over ethernet”) or as a secondary (typically low-speed) signaling circuit.

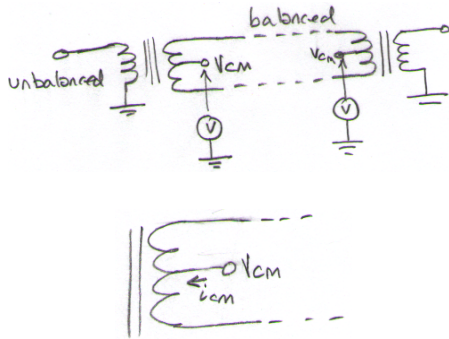

**Exercise 3:** If the common-mode circuit is used to carry 500mA, how much current flows through each half of the transformer secondary? What is the net effect on the flux in the transformer core?

Transformers can also convert impedances. The impedance ratio is the square of the turns ratio while the current ratio is the same as the turns ratio.

Transformers also protect logic circuits against high DC (or low frequency AC) voltages that might be accidentally applied to the transmission line. Each transformer will have a rated maximum isolation between primary and secondary. Typically this is on the order of 1kV or more. The term used for the transformers used for data interfaces such as 100BT Ethernet is “magnetics”.


The main disadvantages of transformers are that (1) they do not pass low frequency or DC signals and that (2) their cost and size remains relatively high because they cannot be integrated into ICs.

## Optoisolators

Optoisolators provide a way of isolating two circuits by coupling via light transmission.

An optoisolator (or optocoupler) consists of an LED and a photodiode in the same package. The input of the optoisolator is the LED. The LED generates light when current flows through it. The light from

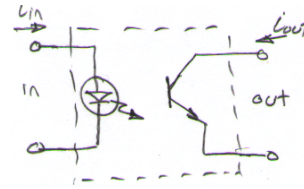the LED shines on a photodiode or phototransistor. The photodiode conducts when light from the LED strikes it. The photodiode is connected to the output circuit.



Since the connection between the LED and photodiode is by light alone, the input and output can be completely isolated electrically. The two sides do not even have to share a ground connection.

**Exercise 4:** When the input to the optocoupler is high, will the output be high or low? Assume a pull-up is connected to the output.