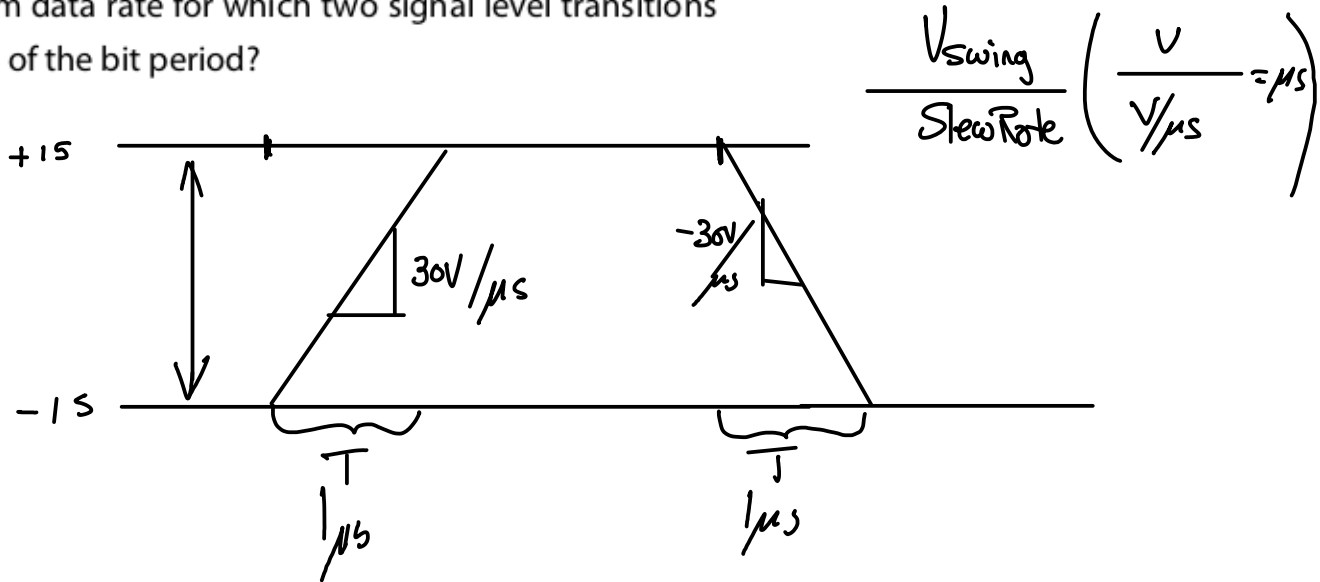


# Lecture 6

**Exercise 1:** The RS-232 standard specifies a maximum slew rate of  $30\text{V}/\mu\text{s}$ . Assuming a voltage swing of 30 volts, what is the maximum data rate for which two signal level transitions occupy 10% of the bit period?




$$1\mu\text{s} + 1\mu\text{s} = 10\% \text{ of } T_{\text{bit}}$$

$$2\mu\text{s} = 0.1 T_{\text{bit}} \quad T_{\text{bit}} = 20\mu\text{s}$$

$$f_{\text{bit}} = \frac{1}{T_{\text{bit}}} \quad f_{\text{bit}} = \frac{1}{20 \times 10^{-6}} = 50 \text{ kHz} = 50 \text{ kb/s}$$

**Exercise 2:** If the common-mode circuit is used to carry 500mA, how much current flows through each half of the transformer secondary? What is the net effect on the flux in the transformer core?

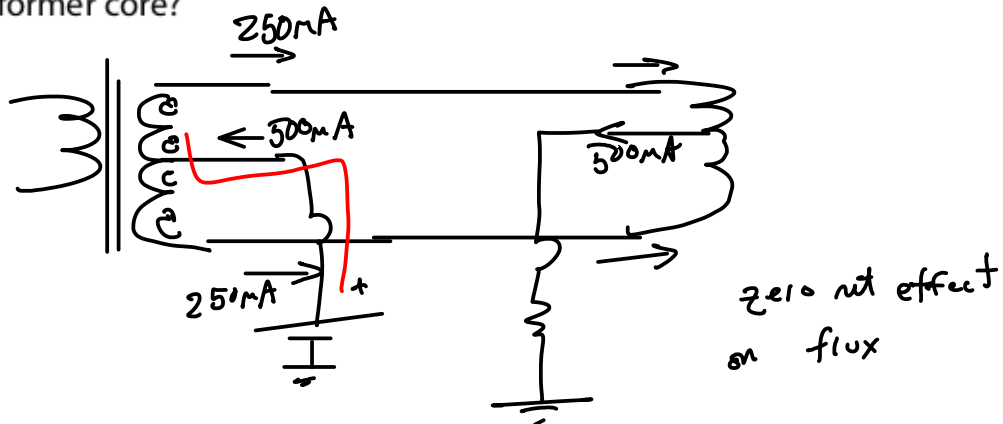

**Exercise 3:** When the input to the optocoupler is high, will the output be high or low? Assume a pull-up is connected to the output.

input high  $\rightarrow$  LED ON  
LED ON  $\rightarrow$  photo transistor on  
transistor on  $\rightarrow$  output pulled low.