

Solution to Assignment 3

RTL Design

Question 1

The cputypes Package

This package defines the types and constants that are used throughout the design.

```
library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_arith.all ;

package cputypes is

    -- memory words
    subtype dword is unsigned (7 downto 0) ;
    subtype iword is std_logic_vector (7 downto 0) ;

    -- addresses (5-bit)
    subtype addr is unsigned (4 downto 0) ;

    -- opcodes and codes (cpu and alu use same opcodes)
    subtype opcode is std_logic_vector (2 downto 0) ;
    subtype alu_opcode is std_logic_vector (2 downto 0) ;
    subtype pc_opcode is std_logic_vector (1 downto 0) ;

    constant load : opcode := "000" ;
    constant store : opcode := "001" ;
    constant loadi : opcode := "010" ;
    constant addop : opcode := "011" ;
    constant notop : opcode := "100" ;
    constant andop : opcode := "101" ;
    constant jz : opcode := "110" ;
    constant jn : opcode := "111" ;

    constant hold : pc_opcode := "00" ;
    constant incr : pc_opcode := "01" ;
    constant jump : pc_opcode := "10" ;

end cputypes;
```

Instruction Memory ROM

```
-- ELEC 379 Assignment 3 Solutions
-- Ed Casas, October 9, 1998
-- Instruction Memory ROM
-- size: 32x8
-- contents: sample program

library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_arith.all ;

use work.cputypes.all ;
```

```
entity rom is
    port (
        address : in addr ;
        instr : out iword
    ) ;
end rom ;

architecture rtl of rom is
begin
    with conv_integer(address) select instr <=
        "01000000" when 0, -- LOADI 0
        "00100000" when 1, -- STORE 0
        "01000001" when 2, -- LOADI 1
        "00100001" when 3, -- STORE 1
        "01000010" when 4, -- LOADI 2
        "10000000" when 5, -- NOT
        "01100001" when 6, -- ADD 1
        "11100110" when 7, -- JN 6
        "11001000" when 8, -- JZ 8
        "00000000" when others ;
end rtl ;
```

The select expression should have been a 5-bit-wide type instead of integer to ensure that the synthesizer did not generate 32-bit logic (which is the normal width for the integer type). Figure 1 shows the simulation results.

Data Memory RAM

```
library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_arith.all ;
use work.cputypes.all ;

entity ram is
    port (
        din : in dword ;
        a : in addr ;
        write, clk : in std_logic ;
        d_out : out dword
    ) ;
end ram ;

architecture rtl of ram is
    type dataarray is array (31 downto 0) of dword ;
    signal ramarray : dataarray ;
    signal d, nextd : dword ;
begin
    -- output value is the indexed array element
    d <= ramarray (conv_integer(unsigned(a))) ;
```

 


Figure 1: Simulation Results for Instruction ROM.

```

-- next value of the indexed array element
nextd <= din when write = '1' else d ;

-- register the indexed array element
process(clk)
begin
    if clk'event and clk = '1' then
        ramarray(conv_integer(unsigned(a)))
            <= nextd ;
    end if ;
end process ;

d_out <= d ;
end rtl ;

std_logic_vector(a)    when notop,
unsigned(std_logic_vector(d) and
std_logic_vector(a))  when andop,
a                      when others ;

-- zero and negative flags from accumulator
zero <=
    '1' when a = 0 else
    '0' ;

negative <= a(7) ;

-- accumulator register
process(clk)
begin
    if clk'event and clk = '1' then
        a <= nexta ;
    end if ;
end process ;

a_out <= a ;
end rtl ;

```

Figure 2 shows the simulation results.

ALU

The accumulator register datapath is often called the ALU (arithmetic and logic unit).

```

-- ELEC 379 Assignment 3 Solutions
-- Ed Casas, October 9, 1998
-- ALU Datapath

library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_arith.all ;

use work.cputypes.all ;

entity alu is
    port (
        d : in dword ;           -- addressed RAM data
        ia : in addr ;          -- address field
        op : in alu_opcode ;    -- alu operation
        clk : in std_logic ;    -- clock
        a_out : out dword ;     -- current accumulator
        zero, negative : out std_logic -- result flags
    ) ;
end alu ;

architecture rtl of alu is
    signal a, nexta : dword ;
begin
    -- ALU operations
    with op select nexta <=
        d                when load,
        unsigned("000" & ia) when loadi,
        d + a            when addop,
        unsigned(not

```

Figure 3 shows the simulation results.

Program Counter

```

-- ELEC 379 Assignment 3 Solutions
-- Ed Casas, October 9, 1998
-- PC Datapath
-- implements PC load, hold, increment and reset

library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_arith.all ;

use work.cputypes.all ;

entity pc is
    port (
        ia : in addr ;          -- instruction address
        op : in pc_opcode ;     -- opcode
        reset : in std_logic ;
        clk : in std_logic ;
        pc_out : out addr       -- current program counter
    ) ;
end pc ;

architecture rtl of pc is
    signal pc, nextpc, nextaddr : addr ;
begin
    -- next PC value if not reset
    with op select nextaddr <=
        pc + 1 when incr,
        ia    when jump,

```

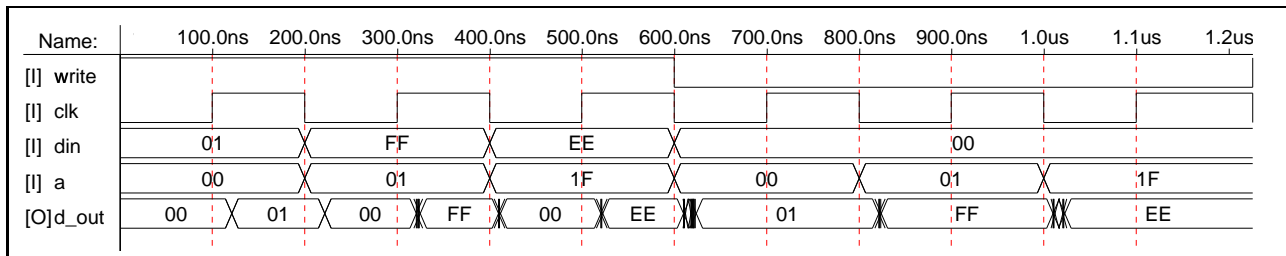


Figure 2: Simulation Results for Data RAM.

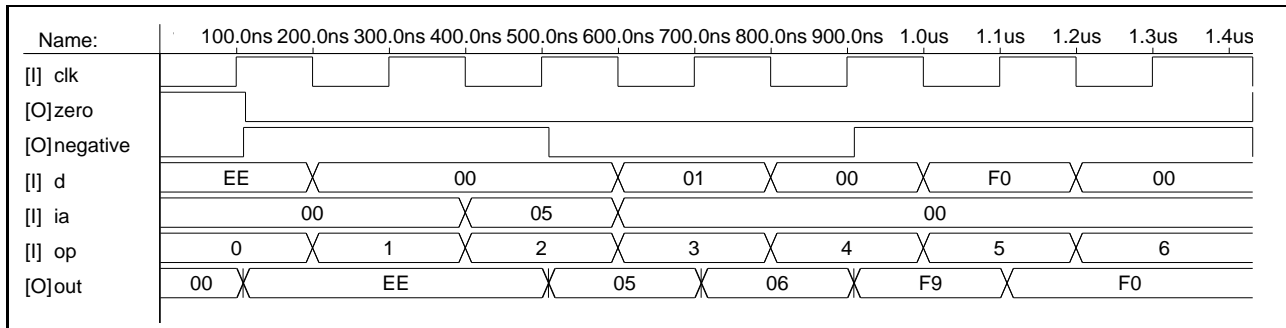


Figure 3: Simulation Results for Accumulator Datapath (ALU).

```

pc      when others ;

-- next PC value
nextpc <=
  conv_unsigned(0,addr'length) when
    reset = '1' else
  nextaddr ;

-- register PC
process(clk)
begin
  if clk'event and clk = '1' then
    pc <= nextpc ;
  end if ;
end process ;

pc_out <= pc ;
end rtl ;

use work.cputypes.all ;

entity decoder is
  port (
    instr : in iword ;           -- instruction
    zero, negative : in std_logic ; -- zero/neg. flags
    aluop : out opcode ;         -- ALU operation
    pcop : out pc_opcode ;       -- PC operation
    write : out std_logic ;      -- RAM write
  ) ;
end decoder ;

architecture rtl of decoder is
  signal op : opcode ;

begin

  -- extract opcode field
  op <= instr(7 downto 5) ;

  -- ALU opcode is same as instruction opcode
  aluop <= op ;

  -- with single-cycle instruction execution the
  -- PC opcode is either load (for branch) or
  -- increment
  pcop <=
    jump when ( op = jz and zero = '1' ) else
    jump when ( op = jn and negative = '1' ) else
    incr ;

  -- write only active for 'store'
  write <= '1' when op = store else '0' ;

end rtl ;

-- ELEC 379 Assignment 3 Solutions
-- Ed Casas, October 9, 1998
-- Controller (Instruction Decoder)
-- Executes one instruction per clock cycle

library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_arith.all ;

```

Figure 4 shows the simulation results.

Instruction Decoder

 


Figure 4: Simulation Results for Program Counter Datapath.

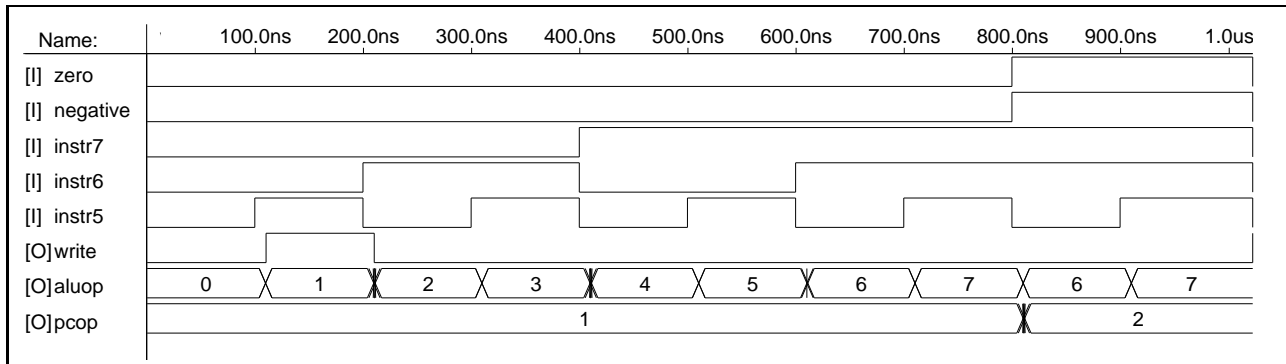


Figure 5: Simulation Results for Instruction Decoder.

Figure 5 shows the simulation results.

The `cpucomponents` Package

This package declares components for the above entities so they can be instantiated in the top-level architecture.

```
library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_arith.all ;
```

```
use work.cputypes.all ;
```

```
package cpucomponents is
```

```
-- RAM
```

```
component ram
  port (
    din : in dword ;
    a : in addr ;
    write, clk : in std_logic ;
    d_out : out dword
  ) ;
end component ;
```

```
-- ROM
```

```
component rom
```

```
  port (
    address : in addr ;
    instr : out iword
  ) ;
end component ;

-- alu
component alu
  port (
    d : in dword ;           -- addressed RAM data
    ia : in addr ;          -- instruction address
    op : in alu_opcode ;    -- alu operation (=opcode)
    clk : in std_logic ;    -- clock
    a_out : out dword ;     -- current accumulator
    zero, negative : out std_logic -- flags
  ) ;
end component ;

-- pc
component pc
  port (
    ia : in addr ;         -- instruction address
    op : in pc_opcode ;   -- opcode
    reset : in std_logic ;
    clk : in std_logic ;
    pc_out : out addr     -- current program counter
  ) ;
end component ;

-- decoder
```

```

component decoder
  port (
    instr : in iword ;           -- instruction
    zero, negative : in std_logic ; -- flags
    aluop : out opcode ;        -- ALU operation
    pcop : out pc_opcode ;      -- PC operation
    write : out std_logic       -- RAM write
  ) ;
end component ;

end rtl ;
end cpucomponents ;

```

Figure 6 shows the simulation results.

Computer

This is the top level of the design. It instantiates the above entities.

```

-- ELEC 379 Assignment 3 Solutions
-- Ed Casas, October 9, 1998
-- Simple Computer Assignment (top-level)

library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_arith.all ;

use work.cputypes.all ;
use work.cpucomponents.all ;

entity cpu is
  port (
    reset, clk : in std_logic ;   -- reset / clock
    pc_out : out addr ;           -- PC (for test)
    instr_out : out iword ;       -- instruction (")
    acc_out : out dword           -- accumulator (")
  ) ;
end cpu ;

architecture rtl of cpu is
  signal ip : addr ;             -- from PC
  signal instr : iword ;        -- from ROM
  signal ramout : dword ;       -- from RAM
  signal acc : dword ;          -- from ALU
  signal zero, negative : std_logic ;
  signal aluop : alu_opcode ;   -- from controller
  signal pcop : pc_opcode ;
  signal write : std_logic ;

  signal add : addr ;           -- address field

begin
  -- extract address field from current instruction
  add <= unsigned(instr(4 downto 0)) ;

  -- computer components
  pcl: pc    port map ( add, pcop, reset, clk, ip ) ;

  rom1: rom  port map ( ip, instr ) ;

  ram1: ram  port map ( acc, add, write, clk, ramout ) ;

  alu1: alu  port map ( ramout, add, aluop, clk, acc,
    zero, negative ) ;

  decoder1:
    decoder port map ( instr, zero, negative,
      aluop, pcop, write ) ;

```

 


Figure 6: Simulated Execution of Sample Program.