

# VHDL for Complex Designs


*This lecture introduces some aspects of VHDL that are useful when designing complex logic circuits. After this lecture you should be able to:*

- *make library packages visible*
- *declare components and save them in packages*
- *instantiate components into an architecture*
- *declare `std_logic`, `std_logic_vector`, `signed` and `unsigned` signals*
- *declare enumerated types and subtypes of array types and save them in packages*
- *use conditional signal assignments*
- *instantiate tri-state outputs*
 
## Libraries, Packages and Components

When designing complex logic circuits it's desirable to decompose the design into simpler parts. Each of these parts can be written and tested separately, perhaps by different people. If the parts are sufficiently general then it might also be possible to re-use them in future projects.

Re-use in VHDL is done by saving these parts (called "components") in "packages". A package typically contains a set of components for a particular application. Packages are themselves stored in "libraries":



To make the components in a package available ("visible") in another design, we use `library` statements to specify the libraries to be searched and a `use` statement for each package we wish to use. The two most commonly used libraries are called `IEEE` and `WORK`.

In the Max+PlusII VHDL implementation a library is a directory and each package is a file in that directory. The package file is a database containing information about the components in the package (the component inputs, outputs, types, etc).

The `WORK` library is always available without hav-

ing to use a library statement. It is simply the current project directory.

`library` and `use` statements must be used before *each* design unit (entity or architecture) that makes use of components found in those packages. For example, if you wanted to use the `numeric_bit` package in the `ieee` library you would use:

```
library ieee ;
use ieee.numeric_bit.all ;
```

and if you wanted to use the `dsp` package in the `WORK` library you would use:

```
use work.dsp.all ;
```

Exercise: Why is there no `library` statement in the second example?

## Creating Components

To create components we put component declarations within a package declaration. When we compile the file the information about the components in the package are saved in a file with the name of the package in the `WORK` library. The components in the package can then be used in other designs by making them visible with a `use` statement.

A component declaration is similar to an entity declaration and simply defines the input and output

signals. Note that a component declaration does not create hardware – only when the component is used in an architecture is the hardware generated (“instantiated”).

For example, the following code creates a package called `flipflops` containing only one component called `rs` with inputs `r` and `s` and an output `q` when it is analyzed:

```
package flipflops is
  component rs
    port ( r, s : in bit ; q : out bit ) ;
  end component ;
end flipflops ;
```

Exercise: If you analyzed this code, what file would be created? Where would it be placed?

## Component Instantiation

Once a component has been placed in a package, it can be used (“instantiated”) in an architecture. A component instantiation simply describes how the component is “hooked up” to the other signals in the architecture. It is thus a *concurrent* statement like the process statement rather than a *sequential* statement and a component instantiation cannot be put inside a process.

The following example shows how 2-input exclusive-or gates can be used to built a 4-input parity-check circuit using component instantiation. This type of description is called *structural VHDL* because we are defining the structure rather than the behaviour of the circuit.

There are two files: the first file describes the `xor2` component (although a typical package defines more than one component):

```
-- define an xor2 component in a package

package xor_pkg is
  component xor2
    port ( a, b : in bit ; x : out bit ) ;
  end component ;
end xor_pkg ;
```

the second file describes the `parity` entity that uses the `xor2` component:


```
-- parity function built from xor gates
```

```
use work.xor_pkg.all ;

entity parity is
  port ( a, b, c, d : in bit ; p : out bit ) ;
end parity ;

architecture rtl of parity is
  -- internal signals
  signal x, y : bit ;
begin
  x1: xor2 port map ( a, b, x ) ;
  x2: xor2 port map ( c, x, y ) ;
  x3: xor2 port map ( d, y, p ) ;
end rtl ;
```

 The resulting top-level schematic for the `parity` entity is:



Exercise: Label the connections within the parity generator schematic with the signal names used in the architecture.

Although components don’t necessarily have to be created using VHDL descriptions, we could have done so by using the following entity/architecture pair:

```
-- xor gate

entity xor2 is
  port ( a, b : in bit ; x : out bit ) ;
end xor2 ;

architecture rtl of xor2 is
begin
  process(a,b)
  begin
    x <= a xor b ;
  end process ;
end rtl ;
```

## Type Declarations

It’s often useful to make up new types of signals for a project. We can do this in VHDL by including type declarations in packages. The two most common uses for defining new types are to declare arrays of given dimensions (e.g. a bus of a given width) and to declare types that can only have one of a set of possible values (called enumeration types).

The following example shows how a package called `dsp_types` that declares two new types is created:

```

package dsp_types is
  type mode is (slow, medium, fast) ;
  subtype sample is bit_vector (7 downto 0) ;
end dsp_types ;

```

Note that we need to use a subtype declaration in the second example because the `bit_vector` type is already defined. Type declarations are often placed in packages to make them available to multiple design units.

## std\_logic Packages

In the IEEE library there are two packages that are often used. These packages define alternatives to the `bit` and `bit_vector` types for logic design.

The first package, `std_logic_1164`, defines the types `std_logic` (similar to `bit`) and `std_logic_vector` (similar to `bit_vector`). The advantage of the `std_logic` types is that they can have values other than '0' and '1'. For example, an `std_logic` signal can also have a high-impedance value ('Z'). The `std_logic_1164` package also re-defines ("overloads") the standard boolean operators so that they also work with `std_logic` signals.

The second package is called `std_logic_arith`<sup>1</sup> and defines the types `signed` and `unsigned`. These are subtypes of `std_logic_vector` with overloaded operators that allow them to be used as both vectors of logic values and as binary values (in two's complement or unsigned representations). Although the standard arithmetic operators (+, -, \*, /, \*\*) can be applied to signals of type `signed` or `unsigned`, it may not be practical or possible to synthesize complex operators such as multiplication, division or exponentiation.

For example, we could generate the combinational logic to build a 4-bit adder using the following architecture:

```

library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_arith.all ;

entity adder4 is
  port (
    a, b : in unsigned (3 downto 0) ;
    c : out unsigned (3 downto 0) ) ;

```

<sup>1</sup>The IEEE standard is really `numeric_std` but it's not widely used yet.


```

end adder4 ;

architecture rtl of adder4 is
begin
  c <= a + b ;
end rtl ;

```

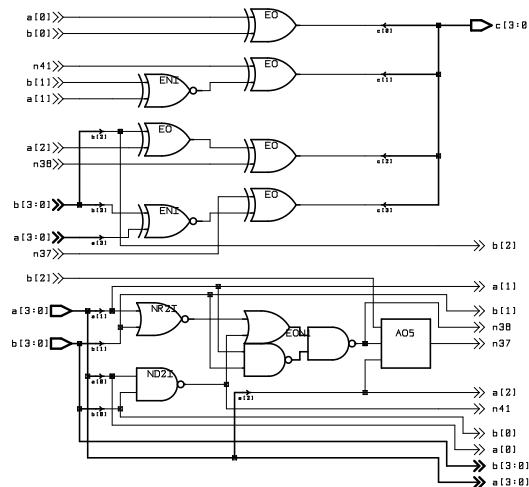The resulting (rather messy) schematic is:



## Conditional Assignment

In the same way that a selected assignment statement models a case statement in a sequential programming language, a conditional assignment statement models an if/else statement. Like the selected assignment statement, it is also a *concurrent* statements.

For example, the following circuit outputs the position of the left-most '1' bit in the input:

```

library ieee ;
use ieee.std_logic_1164.all ;


entity nbits is port (
  b : in std_logic_vector (3 downto 0) ;
  n : out std_logic_vector (2 downto 0) ) ;
end nbits ;

architecture rtl of nbits is
begin
  n <=
    "100" when b(3) = '1' else
    "011" when b(2) = '1' else
    "010" when b(1) = '1' else
    "001" when b(0) = '1' else
    "000" ;
end rtl ;

```

Note that the conditions are tested in the order that they appear in the statement and only the first value whose controlling expression is true is assigned.

The resulting schematics is:

 

## Tri-State Buses

A tri-state output can be set to the normal high and low logic levels as well as to a high-impedance state. This type of output is often used where different devices must drive a bus at different times. One way to specify to the VHDL synthesizer that an output should be set to the high-impedance state is to use a signal of `std_logic` type and assign it a value of 'Z'.

The following example shows an implementation of a 4-bit buffer with an enable output. When the enable is not asserted the output is in high-impedance mode :

```

library ieee ;
use ieee.std_logic_1164.all ;

entity tbuf is port (
  d : in std_logic_vector (3 downto 0) ;
  q : out std_logic_vector (3 downto 0) ;
  en : in std_logic
) ;
end tbuf ;

architecture rtl of tbuf is
begin
  q <=
    d when en = '1' else
    "ZZZZ" ;
end rtl ;

```

The resulting schematic for the tbuf is:

