

Mid-Term Exam Solutions

Question 1

The simplest solution uses the approach described in the hints: an unsigned 9-bit value is incremented on each clk rising edge and is reset when the tdc signal is asserted. The spark output is a combinational function of the hispeed input and the angle. The schematic generated for this architecture by Synopsys' *Design Compiler* is shown in Figure 1.

```

library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_arith.all ;

entity ignition is
    port (
        clk : in std_logic ;
        tdc, hispeed : in std_logic ;
        spark : out std_logic ) ;
end ignition ;

architecture rtl of ignition is
    signal angle, nextangle : unsigned (8 downto 0) ;
begin
    -- crankshaft angle counter
    nextangle <=
        conv_unsigned(0,9) when tdc = '1' else
        angle + conv_unsigned(1,9) ;

    process(clk)
    begin
        if clk'event and clk = '1' then
            angle <= nextangle ;
        end if ;
    end process ;

    -- spark output
    spark <=
        '1' when (
            hispeed = '1' and
            angle >= conv_unsigned(355,9) and
            angle <= conv_unsigned(359,9) ) else
        '1' when (
            hispeed = '0' and
            angle >= conv_unsigned(0,9) and
            angle <= conv_unsigned(4,9) ) else
        '0' ;
end rtl ;

```

Although this solution is acceptable, it has three flaws: (1) if the hispeed input changes while the angle is between 355 and 4 degrees the output would not correspond to either of the desired outputs, (2) the output is not registered and thus will contain

glitches, and (3) the use of arithmetic comparisons will probably result in an implementation requiring four 9-bit comparators. A better solution requires registering the hispeed input before it is used, registering the spark output and using a state machine instead of arithmetic comparisons:

```

architecture rtl of ignition is
    signal advance, nextadvance : std_logic ;
    signal ospark, nextospark : std_logic ;
    signal angle, nextangle : unsigned (8 downto 0) ;
begin
    -- crankshaft angle counter
    nextangle <=
        conv_unsigned(0,9) when tdc = '1' else
        angle + conv_unsigned(1,9) ;

    process(clk)
    begin
        if clk'event and clk = '1' then
            angle <= nextangle ;
        end if ;
    end process ;

    -- latch 'hispeed' as 'advance' at 354 degrees
    nextadvance <=
        hispeed when angle = conv_unsigned(353,9) else
        advance ;

    process(clk)
    begin
        if clk'event and clk = '1' then
            advance <= nextadvance ;
        end if ;
    end process ;

    -- spark output state machine
    nextospark <=
        '1' when advance = '1' and
        angle = conv_unsigned(354,9) else
        '0' when advance = '1' and
        angle = conv_unsigned(359,9) else
        '1' when advance = '0' and
        angle = conv_unsigned(359,9) else
        '0' when advance = '0' and
        angle = conv_unsigned( 4,9) else
        ospark ;

    process(clk)
    begin
        if clk'event and clk = '1' then
            ospark <= nextospark ;
        end if ;
    end process ;

    -- registered spark control output
    spark <= ospark ;

```

 


Figure 1: Simple Solution for Question 1.

```
end rtl ;
```

Which results in the simpler and more reliable design shown in Figure 2.

Question 2

```
;
; copy 64-byte buffer at C4000H to port 220H
; ELEC 379 Mid-Term Exam Question 2
; Ed Casas, 1998/11/26
;

copyout:
    push ax      ; save working registers
    push bx
    push cx
    push dx
    push ds

    mov  ax,c400  ; DS:AX points to buffer
    mov  ds,ax
    mov  bx,0

loop:
```

```

    mov  al,[bx]  ; get byte from buffer
    mov  cl,220  ; write to O/P port
    out  cl,al
    add  bx,1      ; point to next byte
    cmp  bx,64    ; repeat 64 times
    jnz  loop
    pop  ds      ; restore registers
    pop  dx
    pop  cx
    pop  bx
    pop  ax
    ret

```

Question 3

- (a) The 12 LS bits ($4kB = 2^{10} \times 2^2$) are used to select a byte within the 4 kB region, so the decoder uses the $(16 - 12 = 4)$ MS bits. The MS 4 bits of the start address, $4000H$, are 0100. The answer is:

 


Figure 2: Improved Solution for Question 1.

```

en <=
  '0' when a(15 downto 12) = "0100" else
  '1' ;

```

- (b)** The `mov [45],ax` instruction stores two bytes starting at location 45, so locations 45 and 46 will be altered.

The 80386SX CPU has a 16-bit data bus which allows simultaneous access to two bytes if they are at an even/odd address pair. However, address 45 is the MS byte of the word at address 44/45, while byte 46 is the LS byte of the word at address 46/47, so the CPU will execute two write cycles to execute these instructions.

The Intel 80x86 processors store multi-byte values in little-endian order so location 45 will be set to the LS byte, 34H and location 46 will be set to the MS byte, 12H.

The last instruction loads AL, the LS 8 bits of

AX, with the value at location 46, 12. The final value in AX is thus 1212H.

- (c)** The two choices for RAM are SRAM and DRAM. SRAM, although more expensive on a per-bit basis, has faster access times and does not require complex refresh circuitry. For a small and fast memory system SRAM would be the better choice.