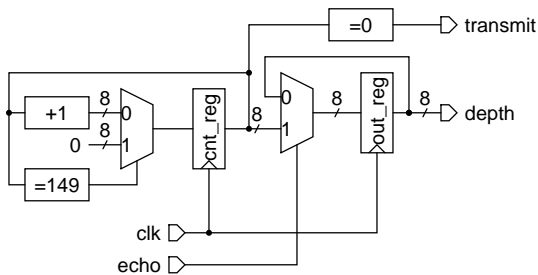


Solutions for Mid-Term Exam

Question 1

The solution consists of two registers: one to implement a counter and one to load and hold the count when the echo signal is asserted. The counter register must be 8 bits wide to be able to count up to 150 ($2^7 = 128$ and $2^8 = 256$). The counter is reset to 0 after it reaches 149 so that the counter period is 150 clock cycles. The transmit output is simply a signal that decodes a zero count. This output should really be registered to avoid glitches. The following block diagram shows the solution:



Which could be described in VHDL as:

```
-- EECE 379 1999/2000 Term 2
-- Mid-Term Exam, Question 1
-- Ed Casas, 2000/2/28

library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_arith.all ;

entity sounder is
    port ( clk, echo : in std_logic ;
          transmit : out std_logic ;
          depth : out unsigned (7 downto 0) ) ;
end sounder ;

architecture rtl of sounder is
    signal cntreg, next_cntreg : unsigned (7 downto 0) ;
    signal outreg, next_outreg : unsigned (7 downto 0) ;
begin
    -- counter counts from 0 to 149
    next_cntreg <=
        conv_unsigned(0,8) when cntreg = 149 else
        cntreg + 1 ;

    -- outreg loads/holds count when echo returns
    next_outreg <=
        cntreg when echo = '1' else
        outreg ;
```

```
-- register count and output
process(clk)
begin
    if clk'event and clk='1' then
        cntreg <= next_cntreg ;
        outreg <= next_outreg ;
    end if ;
end process ;

-- generate transmit pulse for one clock period
transmit <=
    '1' when cntreg = 0 else
    '0' ;

-- connect output
depth <= outreg ;
```

end rtl ;

Figure 1 show the simulation results.

Question 2

There are many possible solutions. A solution written in C could be as follows:

```
/*
EECE379 1999/2000 Term 2
Mid-Term exam Solutions
C solution for Question 2
*/

/* Return a non-zero value if the headlight switch is on, zero
otherwise. */

int switch()
{
    return inb(0x300) & 0x80 ;
}

/* Return a non-zero value if the clock signal is '1', zero
otherwise. */

int clock()
{
    return inb(0x300) & 0x01 ;
}

/* Turn the headlight on if 'on' is non-zero, off otherwise. */

void setlights(int on)
{
    outb(0x300,on?1:0) ;
}
```

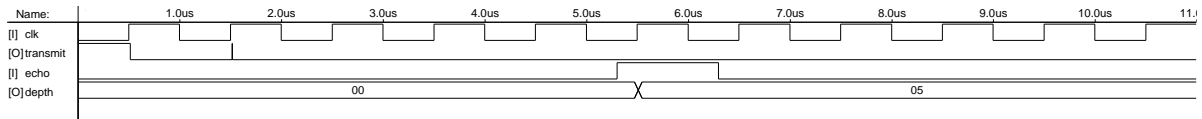


Figure 1: Simulation output.

```

main()                                jge    end_delay
{
  int i, prev ;                        call   clock      ; prev=clock()
                                        mov    prev,al
  while (1) {                          /* loop forever */
    off:                                wait:  call   clock      ; while clock() == prev
      setlights(0) ;                    /* turn lights off */      cmp    al,prev
      while ( ! swtch() ) ;            /* wait until switched on */  je     end_wait
    on:                                  call   switch     ; if switch() goto on
      setlights(1) ;                    /* turn lights on */        jnz   on
      while ( swtch() ) ;              /* wait until switched off */ jmp    wait
                                        end_wait:
    for ( i=0 ; i<30 ; i++ ) { /* delay 30 s */
      prev = clock() ;                /* get initial clock */      mov    ax,count    ; count++
      while ( clock() == prev ) { /* wait for change */
        if ( swtch() ) goto on ; /* check for on */
      }
      jmp delay
    }
                                        end_delay:
  }
                                        jmp    start
}
                                        switch:  ; return switch state
                                        mov    dx,300h
                                        in     al,dx
                                        and    ax,80h
                                        ret
                                        clock:  ; return clock signal
                                        mov    dx,300h
                                        in     al,dx
                                        and    ax,01h
                                        ret
                                        set:    ; turn lights on/off
                                        mov    dx,300h
                                        out   dx,al
                                        ret
                                        count  dw    1 dup (?) ; delay count
                                        prev   db    1 dup (?) ; previous port value
                                        code ends
                                        end    start

```

Which could be written in assembler as follows.
 The comments are references to the C version (rather than following good commenting style).

```

code segment public
  assume cs:code,ds:code
  org 100h
start:
off:  mov  al,0      ; set(0)
      call set
off1: call  switch   ; while ! switch()
      jz  off1
on:   mov  al,1      ; set(1)
      call set
on1:  call  switch   ; while switch()
      jnz on1
      mov ax,0      ; count=0
      mov count,ax
delay: mov ax,count  ; while count < 30
      cmp ax,30

```