

Solution to Assignment 1

Question 1

A possible solution is shown below. An if/else statement is used to model the output enables and a case statement is used to set the outputs.

```
-- ELEC 379 Assignment 1 Solution
-- 74HCA138 3-to-8 decoder
-- Ed Casas, Jan 16 1998


entity MM74HCA138 is port (
    a, b, c : in bit ;
    g1, g2a, g2b : in bit ;
    y : out bit_vector (7 downto 0) ) ;
end MM74HCA138 ;

architecture rtl of MM74HCA138 is
    signal tmp : bit_vector (2 downto 0) ;
begin

    -- build vector so can use case statement
    process(a,b,c)
    begin
        tmp <= a & b & c ;
    end process ;

    process(tmp,g1,g2a,g2b)
    begin
        if g1 = '1' and g2a = '0' and g2b = '0'
        then
            case tmp is
                when "000" => y <= "11111110" ;
                when "001" => y <= "11111101" ;
                when "010" => y <= "11111011" ;
                when "011" => y <= "11110111" ;
                when "100" => y <= "11101111" ;
                when "101" => y <= "11011111" ;
                when "110" => y <= "10111111" ;
                when "111" => y <= "01111111" ;
            end case ;
        else
            y <= "11111111" ;
        end if ;
    end process ;

end rtl ;
```

 

The resulting schematic is: