

# Solution to Assignment 3

## RTL Design

### Question 1

#### The cputypes Package

This package defines the types and constants that are used throughout the design.

```
-- ELEC 379 Assignment 3 Solutions
-- Ed Casas, March 2, 1999
-- CPU Types

library ieee ;
use ieee.std_logic_1164.all ;

package cputypes is

    -- memory words
    subtype word is std_logic_vector (7 downto 0) ;

    -- addresses
    subtype address is std_logic_vector (4 downto 0) ;

    -- opcodes
    subtype opcode is std_logic_vector (2 downto 0) ;

    constant load_op   : opcode := "000" ;
    constant store_op  : opcode := "001" ;
    constant add_op    : opcode := "010" ;
    constant sub_op    : opcode := "011" ;
    constant jmp_op    : opcode := "100" ;
    constant jnz_op    : opcode := "101" ;
    constant jn_op     : opcode := "110" ;

    -- datapath operations
    type alu_opcode is ( hold, load, add, sub ) ;
    type i_opcode is ( hold, load ) ;
    type pc_opcode is ( hold, load, incr, clear ) ;

end cputypes;
```

#### Memory

```
-- ELEC 379 Assignment 3 Solutions
-- Ed Casas, March 2, 1999
-- Memory

library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_arith.all ;
use work.cputypes.all ;

entity memory is
    port (
```

```
        addr : in address ;
        data_out : out word ;
        data_in : in word ;
        write, clk : in std_logic
    );
end memory ;

architecture rtl of memory is
    type dataarray is array (15 downto 0) of word ;
    signal ram_data : dataarray ;
    signal ram_out, next_ram_out, rom_out : word ;
    signal ram_enable : std_logic ;
    signal addr_low : unsigned(address'left-1 downto 0) ;
begin
    -- RAM is upper half
    ram_enable <= addr(address'left) ;

    -- LS bits of address
    addr_low <= unsigned(addr(address'left-1 downto 0)) ;

    -- ROM contains the program
    with addr_low select rom_out <=
        "00000111" when "0000",
        "00110000" when "0001",
        "00000110" when "0010",
        "01110000" when "0011",
        "10100011" when "0100",
        "10000101" when "0101",
        "00000011" when "0110",
        "00000001" when "0111",
        "00000000" when others ;

    -- RAM output value is the indexed array element
    ram_out <=
        ram_data (conv_integer(addr_low)) ;

    -- next value to be stored in RAM
    next_ram_out <=
        data_in when write = '1' and ram_enable = '1' else
        ram_out ;

    -- register the indexed array element
    process(clk)
    begin
        if clk'event and clk = '1' then
            ram_data(conv_integer(addr_low)) <=
                next_ram_out ;
        end if ;
    end process ;

    data_out <=
        ram_out when ram_enable = '1' else
        rom_out ;

end rtl ;
```

Figure 1 shows the simulation results.

 


Figure 1: Simulation Results for Memory.

## A Datapath

The accumulator register datapath is often called the ALU (arithmetic and logic unit).

```
-- ELEC 379 Assignment 3 Solutions
-- Ed Casas, March 8, 1998
-- ALU Datapath

library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_arith.all ;
use work.cputypes.all ;

entity alu is
    port (
        a_in : in word ;          -- addressed RAM data
        op : in alu_opcode ;      -- alu operation
        a_out : out word ;        -- current accumulator value
        zero, negative : out std_logic ; -- flags
        clk : in std_logic        -- clock
    );
end alu ;

architecture rtl of alu is
    signal a, nexta : word ;
begin
    -- ALU operations
    with op select nexta <=
        a_in           when load,
        unsigned(a) + unsigned(a_in) when add,
        unsigned(a) - unsigned(a_in) when sub,
        a               when others ;
    -- accumulator register
    process(clk)
    begin
        if clk'event and clk = '1' then
            a <= nexta ;
        end if ;
    end process ;
    a_out <= a ;
    -- zero and negative flags from current accumulator
    zero <=
        '1' when a = "00000000" else
        '0' ;
    negative <= a(word'left) ;
end rtl ;
```

Figure 2 shows the simulation results.

## Instruction Register

```
-- ELEC 379 Assignment 3 Solutions
-- Ed Casas, March 2, 1999
-- Instruction Register Datapath

library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_arith.all ;
use work.cputypes.all ;

entity iregister is
    port (
        i_in : in word ;
        op : in i_opcode ;
        i_out : out word ;
        clk : in std_logic      ) ;
end iregister ;

architecture rtl of iregister is
    signal i, nexti : word ;
begin
    -- next instruction register value if not reset
    with op select nexti <=
        i_in      when load,
        i         when others ;
    -- register I
    process(clk)
    begin
        if clk'event and clk = '1' then
            i <= nexti ;
        end if ;
    end process ;
    i_out <= i ;
end rtl ;
```

Figure 3 shows the simulation results.

## Program Counter

```
-- ELEC 379 Assignment 3 Solutions
-- Ed Casas, March 2, 1999
-- PC Datapath
-- implements PC hold, load, increment and reset

library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_arith.all ;
use work.cputypes.all ;
```

 


Figure 2: Simulation Results for Accumulator Datapath (ALU).

 


Figure 3: Simulation Results for Instruction Register Datapath.

## Instruction Decoder

```

entity pc is
  port (
    pc_in : in address ;      -- instruction address
    op : in pc_opcode ;       -- opcode
    pc_out : out address ;    -- current program counter
    clk : in std_logic
  );
end pc ;

architecture rtl of pc is
  signal pc, nextpc : address ;
begin
  -- next PC value if not reset
  with op select nextpc <=
    pc
    when hold,
    pc_in
    when load,
    unsigned(pc) + 1
    when incr,
    "00000"
    when others ;

  -- register PC
  process(clk)
  begin
    if clk'event and clk = '1' then
      pc <= nextpc ;
    end if ;
  end process ;

  pc_out <= pc ;
end rtl ;

```

```

-- ELEC 379 Assignment 3 Solutions
-- Ed Casas, March 2, 1999
-- Controller (Instruction Decoder)
-- Each instruction takes 2 cycles (fetch, execute)

library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_arith.all ;
use work.cputypes.all ;

entity decoder is
  port (
    clk, reset : in std_logic ;      -- clock and reset
    instr : in opcode ;             -- current instruction
    zero, negative : in std_logic ;  -- flags
    alu_op : out alu_opcode ;       -- A operation
    i_op : out i_opcode ;           -- I operation
    pc_op : out pc_opcode ;         -- PC operation
    fetch_out, write : out std_logic -- control
  );
end decoder ;

architecture rtl of decoder is
  signal fetch, nextfetch : std_logic ;
begin
  -- fetch/execute state machine
  nextfetch <=
    '1' when reset = '1' or fetch = '0' else
    '0' ;

  process(clk)

```

Figure 4 shows the simulation results.

process(clk)

 


Figure 4: Simulation Results for Program Counter Datapath.

```

begin
    if clk'event and clk='1' then
        fetch <= nextfetch ;
    end if ;
end process ;

fetch_out <= fetch ;

-- ALU operation
alu_op <=
    hold when fetch = '1' else
    load when instr = load_op else
    add when instr = add_op else
    sub when instr = sub_op else
    hold ;

-- I operation
i_op <=
    load when fetch = '1' else
    hold ;

-- PC operation
pc_op <=
    clear when reset = '1' else
    hold when fetch = '1' else
    load when
        instr = jmp_op or
        (instr = jnz_op and zero /= '1') or
        (instr = jn_op and negative = '1') else
    incr ;

-- write strobe
write <=
    '0' when fetch = '1' else
    '1' when instr = store_op else
    '0' ;

end rtl ;

```

-- CPU Components

```

library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_arith.all ;
use work.cputypes.all ;

package cputcomponents is

-- memory

component memory
    port (
        addr : in address ;
        data_out : out word ;
        data_in : in word ;
        write, clk : in std_logic
    ) ;
end component ;

-- alu

component alu
    port (
        a_in : in word ;      -- addressed RAM data
        op : in alu_opcode ; -- alu operation
        a_out : out word ;   -- current accumulator value
        zero, negative : out std_logic ; -- flags
        clk : in std_logic   -- clock
    ) ;
end component ;

-- instruction register

component iregister
    port (
        i_in : in word ;
        op : in i_opcode ;
        i_out : out word ;
        clk : in std_logic ) ;
end component ;

-- pc

component pc
    port (
        pc_in : in address ; -- instruction address
        op : in pc_opcode ; -- opcode
        pc_out : out address ; -- current program counter
        clk : in std_logic
    ) ;
end component ;

```

-- ELEC 379 Assignment 3 Solutions  
-- Ed Casas, March 8, 1999

 


Figure 5: Simulation Results for Instruction Decoder.

```
-- decoder

component decoder
  port (
    clk, reset : in std_logic ;      -- clock and reset
    instr : in opcode ;             -- current instruction
    zero, negative : in std_logic ; -- flags
    alu_op : out alu_opcode ;       -- A operation
    i_op : out i_opcode ;           -- I operation
    pc_op : out pc_opcode ;         -- PC operation
    fetch_out, write : out std_logic -- control
  );
end component ;

end cpumodel;
```

## Computer

This is the top level of the design. It instantiates the above entities.

```
-- ELEC 379 Assignment 3 Solutions
-- Ed Casas, October 9, 1998
-- Simple Computer Assignment (top-level)

library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_arith.all ;
use work.cputypes.all ;
use work.cpumodel.all ;

entity cpu is
  port (
    reset, clk : in std_logic ; -- reset and clock
    pc_out_out : out address ; -- current PC
    mem_out_out : out word ;   -- memory output
    alu_out_out : out word     -- alu output
  );
end cpu ;

architecture rtl of cpu is
```

```
signal addr : address ; -- address into memory

signal mem_out, alu_out, i_out : word ;
signal pc_out : address ;
signal alu_op : alu_opcode ;
signal i_op : i_opcode ;
signal pc_op : pc_opcode ;
signal write, zero, negative, fetch : std_logic ;

signal i_out_op : std_logic_vector (2 downto 0) ;
signal i_out_addr : std_logic_vector (4 downto 0) ;
begin
  i_out_op <= i_out (7 downto 5) ;
  i_out_addr <= i_out (4 downto 0) ;

  addr <=
    pc_out when fetch = '1' else
    i_out_addr ;

  m1: memory port map ( addr, mem_out, alu_out,
                        write, clk ) ;

  a1: alu port map ( mem_out, alu_op, alu_out,
                      zero, negative, clk ) ;

  i1: iregister port map ( mem_out, i_op, i_out, clk ) ;

  p1: pc port map ( i_out_addr, pc_op, pc_out, clk ) ;

  d1: decoder port map ( clk, reset, i_out_op, zero,
                        negative, alu_op, i_op, pc_op, fetch, write ) ;

  -- test outputs
  pc_out_out <= pc_out ;
  mem_out_out <= mem_out ;
  alu_out_out <= alu_out ;
```

end rtl ;

Figure 6 shows the simulation results.

 


Figure 6: Simulated Execution of Sample Program.