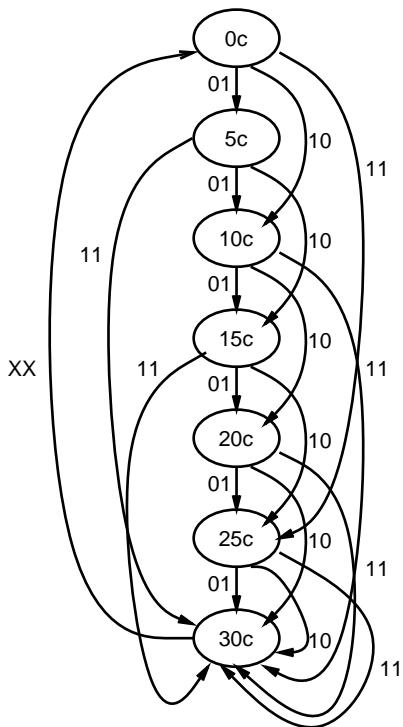


Solutions to Assignment 2

Question 1

The controller inputs are the coin detector outputs (labelled X and Y). The controller output is the candy release signal (labelled R). The seven states correspond to the possible sum of money deposited: 0, 5c, 10c, 15c, 20c, 25c, 30c which are encoded using three state variables (A, B, and C) as 000, 001, 010, 011, 100, 101, and 110. The state transition diagram is:



The tabular description of the state transitions is:

current state <i>ABC</i>	input conditions		next state <i>A'B'C'</i>
	X	Y	
000	0	0	000
000	0	1	001
000	1	0	011
000	1	1	101
001	0	0	001
001	0	1	010
001	1	0	011
001	1	1	110
010	0	0	010
010	0	1	011
010	1	0	100
010	1	1	110
011	0	0	011
011	0	1	100
011	1	0	101
011	1	1	110
100	0	0	100
100	0	1	101
100	1	X	110
101	0	0	101
101	0	1	110
101	1	X	110
110	X	X	000

where X is a “don’t care” condition.

The release is only turned on when the count of money reaches 30 cents. The tabular description of the outputs is:

state	R
0c	0
5c	0
10c	0
15c	0
20c	0
25c	0
30c	1

The next-state equations (not simplified) are:



$$\begin{aligned}
 A' = & \overline{ABC}XY + \overline{ABC}XY + \overline{AB}\overline{C}X\bar{Y} + \overline{AB}\overline{C}XY + \\
 & \overline{ABC}\bar{X}Y + \overline{ABC}\bar{X}\bar{Y} + \overline{ABC}XY + \overline{ABC}\bar{X}Y + \\
 & \overline{ABC}XY + \overline{ABC}X + \overline{ABC}\bar{X}Y + \overline{ABC}\bar{X}Y + \overline{ABC}X
 \end{aligned}$$


$$B' = \overline{ABCX}\bar{Y} + \overline{ABC}\bar{X}Y + \overline{ABCX}\bar{Y} + \overline{ABCXY} + \\ \overline{ABCXY} + \overline{ABCXY} + \overline{ABCXY} + \overline{ABCXY} + \overline{ABCXY} + \overline{ABCXY} + \overline{ABCXY}$$

$$C' = \overline{ABCXY} + \overline{ABCX}\bar{Y} + \overline{ABCXY} + \overline{ABCXY} + \\ \overline{ABCXY} + \overline{ABCXY} + \overline{ABCXY} + \overline{ABCXY} + \overline{ABCXY} + \overline{ABCXY} + \overline{ABCXY}$$


$$R = ABC\bar{C}$$

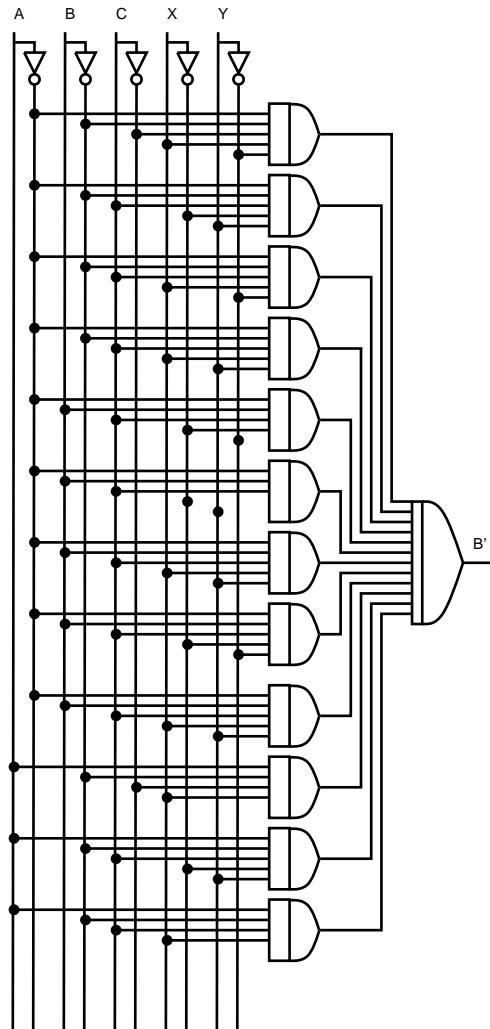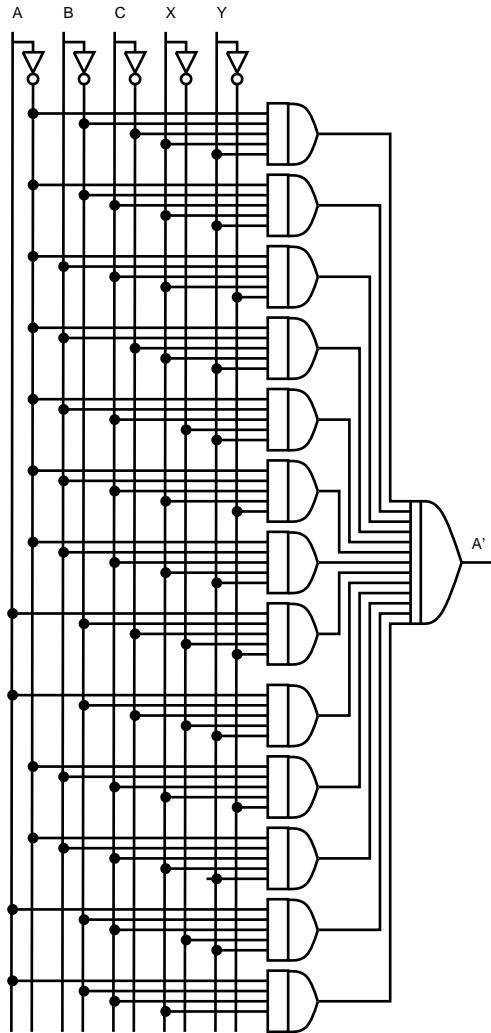Schematic diagrams of the controller implemented directly from the sum-of-products expressions are given below:



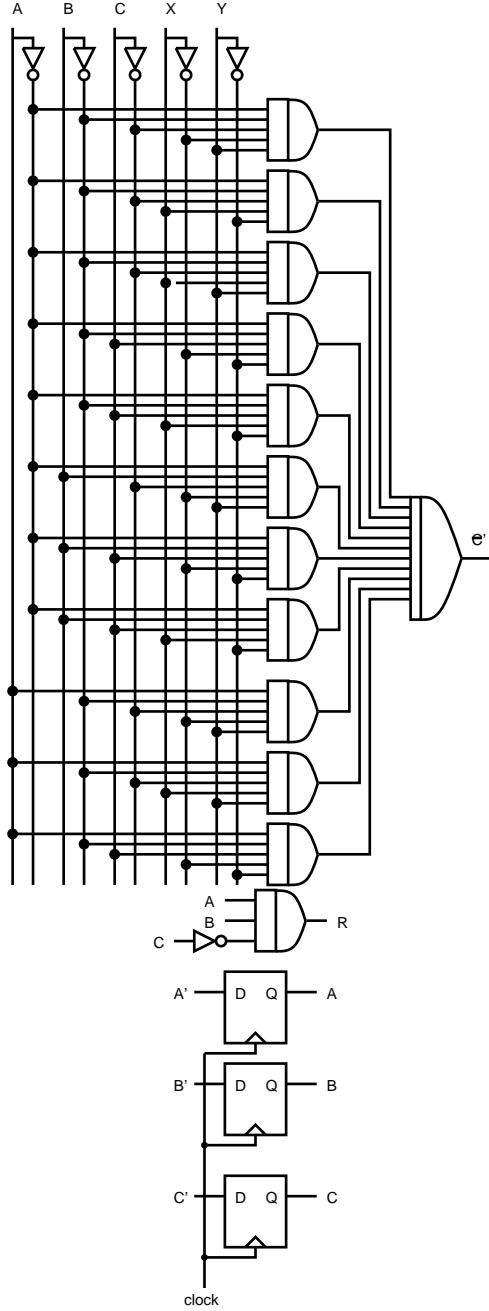

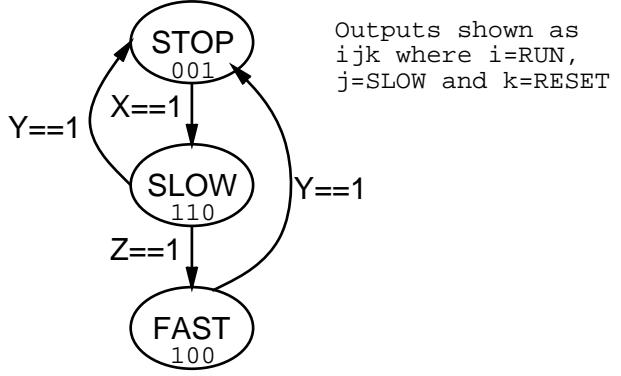In this particular design the candy release signal will be high (equal to one) for one clock period (1 ms).



2. The outputs for each state are:

state	RUN	SLOW	RESET
STOP (00)	0	0	1
SLOW (11)	1	1	0
FAST (10)	1	0	0

where the values after each state name are the binary encodings of the state using two state variables, A and B .

3. A tabular description of the state transition diagram is as follows:

current state	input conditions			next state
	X	Y	Z	
STOP (00)	0	X	X	STOP (00)
STOP (00)	1	X	X	SLOW (11)
SLOW (11)	X	0	0	SLOW (11)
SLOW (11)	X	0	1	FAST (10)
SLOW (11)	X	1	X	STOP (00)
FAST (10)	X	1	X	STOP (00)

4. The sum-of-products boolean expressions for each output signal and for the signal giving the next state are:

$$RUN = A$$

$$SLOW = B$$

$$RESET = \overline{AB}$$

$$A' = \overline{AB}X + AB\overline{Y}$$

$$B' = \overline{AB}X + ABYZ$$

5. a schematic diagram for the controller is:

