


Sequential Logic Design Synthesized Schematics

This page shows the corrected VHDL descriptions and synthesized schematics for the D flip-flop and 2-bit counter.

D Flip-Flop

```
entity D_FF is
    port ( clk, d : in bit ;
          q : out bit ) ;
end D_FF ;

 architecture rtl of D_FF is
begin
    process(clk)
    begin
        if clk'event and clk = '1' then
            q <= d ;
        end if ;
    end process ;
end rtl ;
```



```
        when "11" =>
            nexts <= "00" ;
            count <= "11" ;
        end case ;
    end process ;

    -- sequential logic
    process(clk)
    begin
        if clk'event and clk = '1' then
            current <= nexts ;
        end if ;
    end process ;
end rtl ;
```

2-bit Counter

```
entity count2 is
    port ( clk : in bit ; count :
          out bit_vector (1 downto 0) ) ;
end count2 ;

architecture rtl of count2 is
    signal current, nexts :
        bit_vector (1 downto 0) ;
begin
```

```
    -- combinational logic:
    process(current)
    begin
        -- compute next state and output
        -- from current state and input
        case current is
            when "00" =>
                nexts <= "01" ;
                count <= "00" ;
            when "01" =>
                nexts <= "10" ;
                count <= "01" ;
            when "10" =>
                nexts <= "11" ;
                count <= "10" ;
```

