

Solutions to Assignment 1

VHDL Synthesis

The entity should look something like:


```
-- ELEC 464 Assignment 1
-- model of 74'151 8 to 1 multiplexer with
-- complementary outputs and enable
-- Ed Casas, September 10 1996

entity EC151 is
    port ( a, b, c, s : in bit ;
          d : in bit_vector (7 downto 0) ;
          y, w : out bit ) ;
end EC151 ;
```

A straightforward architecture written with if/then/else statements might look like:

```
architecture rtl of EC151 is
begin
    process(a,b,c,s,d)
    begin
        if s = '0' then
            y <= '0' ;
            w <= '1' ;
        else
            if c='0' and b='0' and a='0' then
                y <= d(0) ;
                w <= not d(0) ;
            elsif c='0' and b='0' and a='1' then
                y <= d(1) ;
                w <= not d(1) ;
            elsif c='0' and b='1' and a='0' then
                y <= d(2) ;
                w <= not d(2) ;
            elsif c='0' and b='1' and a='1' then
                y <= d(3) ;
                w <= not d(3) ;
            elsif c='1' and b='0' and a='0' then
                y <= d(4) ;
                w <= not d(4) ;
            elsif c='1' and b='0' and a='1' then
                y <= d(5) ;
                w <= not d(5) ;
            elsif c='1' and b='1' and a='0' then
                y <= d(6) ;
                w <= not d(6) ;
            else
                y <= d(7) ;
                w <= not d(7) ;
            end if ;
        end if ;
    end process ;
end rtl ;
```

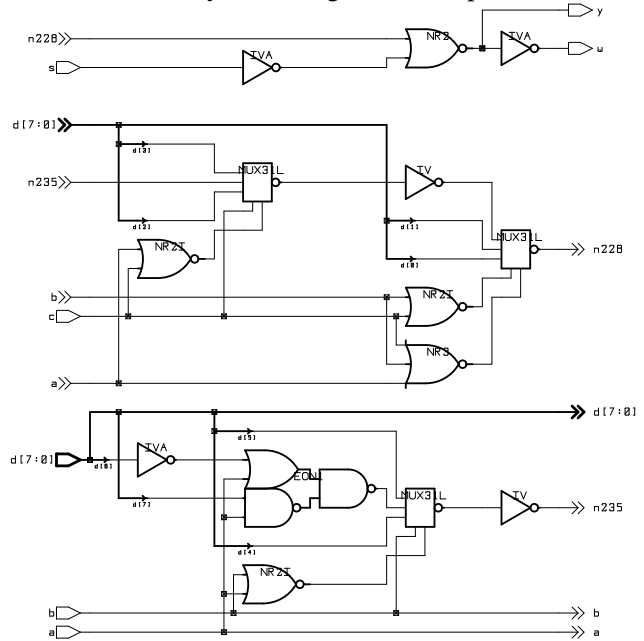The result of synthesizing this description is:



An alternative architecture can be written by deriving the sum-of-products expressions for y and w from a truth table containing all the possible combinations of inputs. The description can be simplified by using a separate process to compute w and y from an intermediate internal signal:

```
architecture rtl of EC151 is
```


```

process(tmp,s)
begin
  y <= s and tmp ;
  w <= not ( s and tmp ) ;
end process ;
end rtl ;

```

Note that the parentheses are required because the and and or logical operators have the same precedence.

 The result of synthesizing this description is:



A third approach is to combine a, b, and c into an internal 3-element bit_vector and use it in a case statement:

```

architecture rtl of EC151 is
  -- internal signals:
  signal tmp : bit ;
  signal sel : bit_vector (2 downto 0) ;
begin

```

This
the pre
The
that we
values
verted
portabl
express
rent sig

```

library
use sy
archite
sig
begin
  tmp
  y <=
  w <=

```

end rtl

This
cuit as
back o
other c
portabl
IEEE \