

Solutions to Assignment 3

Question 1

The following solution uses the high-level design suggested in the assignment. The abbreviation X"nn" allows bit_vector constants to be specified in hexadecimal notation.

```
-- ELEC 464 Assignment 3
-- Ed Casas, September 25 1996

entity snum is
    port ( clk : in bit ;
    a,b,c,d,e,f,g : out bit ) ;

-- pragma dc_script_begin
-- set_port_is_pad "*"
-- set_attribute clk pad_location -type string "P18"
-- set_pad_type -no_clock clk
-- set_attribute a pad_location -type string "P49"
-- set_attribute b pad_location -type string "P48"
-- set_attribute c pad_location -type string "P47"
-- set_attribute d pad_location -type string "P46"
-- set_attribute e pad_location -type string "P45"
-- set_attribute f pad_location -type string "P50"
-- set_attribute g pad_location -type string "P51"
-- pragma dc_script_end

end snum ;

architecture rtl of snum is
    signal i, nexti : bit_vector (3 downto 0) ;
    signal digit : bit_vector (3 downto 0) ;
    signal seg : bit_vector (6 downto 0) ;
begin

    -- counter combinational logic
    process(i)
    begin
        case i is
            when X"0" => nexti <= X"1" ;
            when X"1" => nexti <= X"2" ;
            when X"2" => nexti <= X"3" ;
            when X"3" => nexti <= X"4" ;
            when X"4" => nexti <= X"5" ;
            when X"5" => nexti <= X"6" ;
            when X"6" => nexti <= X"7" ;
            when X"7" => nexti <= X"8" ;
            when X"8" => nexti <= X"0" ;
            when others => nexti <= X"0" ;
        end case ;
    end process ;

    -- counter sequential logic
    process(clk,nexti)
    begin
        if clk'event and clk='0' then
            i <= nexti ;
        end if ;
    end process ;

    -- convert digit index (i) into the i'th digit
    -- of the student number
    process(i)
    begin
        case i is
            when X"0" => digit <= X"F" ;
            when X"1" => digit <= X"8" ;
            when X"2" => digit <= X"7" ;
            when X"3" => digit <= X"6" ;
            when X"4" => digit <= X"5" ;
            when X"5" => digit <= X"4" ;
            when X"6" => digit <= X"3" ;
            when X"7" => digit <= X"2" ;
            when X"8" => digit <= X"1" ;
            when others => digit <= X"F" ;
        end case ;
    end process ;

    -- convert a digit into on/off values for
    -- a 7-segment display
    process(digit)
    begin
        case digit is
            when X"0" => seg <= "1111110" ;
            when X"1" => seg <= "0110000" ;
            when X"2" => seg <= "1101101" ;
            when X"3" => seg <= "1111001" ;
            when X"4" => seg <= "0110011" ;
            when X"5" => seg <= "1011011" ;
            when X"6" => seg <= "1011111" ;
            when X"7" => seg <= "1110000" ;
            when X"8" => seg <= "1111111" ;
            when X"9" => seg <= "1110011" ;
            when others => seg <= "0000000" ;
        end case ;
    end process ;

    -- copy 'seg' vector to individual output ports
    -- need to negate because LED outputs are active-low
    process(seg)
    begin
        a <= not seg(6) ;
        b <= not seg(5) ;
        c <= not seg(4) ;
        d <= not seg(3) ;
        e <= not seg(2) ;
        f <= not seg(1) ;
        g <= not seg(0) ;
    end process ;

end rtl ;

end rtl ;
```