

Solutions to Assignment 1

4.3 and 4.4 Some examples of the code for a four-input XOR function whose input is $a[3:0]$ and whose output is y are:

```
module sillyfunction
  ( input logic [3:0] a,
    output logic y ) ;

`define simplest
`ifdef simple
  assign y = a[3] ^ a[2] ^ a[1] ^ a[0] ;
`elsif forloop
  always_comb begin
    y = '0 ;
    for ( int i=0 ; i<$bits(a) ; i++ )
      y ^= a[i] ;
  end
`elsif simplest
  assign y = ^a ;
`endif
endmodule
```

The modified testbench (with original code shown in comments) is:

```
module testbench3 ;
  logic clk, reset;
  // logic a, b, c, y, yexpected;
  logic [3:0] a ;
  logic y, yexpected;
  logic [31:0] vectornum, errors;
  // logic [3:0] testvectors[10000:0];
  logic [4:0] testvectors[10000:0];

  // instantiate device under test
  // sillyfunction dut(a, b, c, y);
  sillyfunction dut(a, y);

  // generate clock
  always
  begin
    clk = 1; #5; clk = 0; #5;
```

```
    end
    // at start of test, load vectors
    // and pulse reset
    initial
    begin
      // $readmemb("example.tv",
      // testvectors);
      $readmemb("asg1-example.tv",
                testvectors);
      vectornum = 0;
      errors = 0;
      reset = 1;
      #27;
      reset = 0;

    end
    // apply test vectors on rising edge
    // of clk
    always @(posedge clk)
    begin
      #1; // {a, b, c, yexpected}
      // = testvectors[vectornum];
      #1; {a[3], a[2], a[1], a[0],
            yexpected} = testvectors[vectornum];
    end

    // check results on falling edge of clk
    always @(negedge clk)
    if (~reset) begin // skip during reset
      if (y !== yexpected) begin // check result
        // $display("Error: inputs
        // = %b", {a, b, c});
        $display("Error: inputs = %b", a);
        $display(" outputs = %b (%b expected)",
                 y, yexpected);
        errors = errors + 1;
      end
      vectornum = vectornum + 1;
      // if (testvectors[vectornum]
      // === 4'bx) begin
      if (testvectors[vectornum] === 5'bx)
      begin
        $display
          ("%d tests completed with %d errors",
           vectornum, errors);
        $finish;
      end
    end
  endmodule
```

The test vectors for all input combinations and one error is:

```
0000_0
0001_1
0010_1
0011_0
0100_1
0101_0
0110_0
0111_1
1000_1
1001_0
1010_0
1011_1
1100_0
1101_1
1110_1
1111_0
0001_0
xxxx_x
```

The result of running the testbench (with one error) is:

```
# vsim -batch testbench3 -do "run -all"
...
# Loading work.testbench3
# Loading work.sillyfunction
#
# run -all
# Error: inputs = 0001
# outputs = 1 (0 expected)
#      17 tests completed with      1 errors
```

4.22 The code and testbench is:

```
module thermometer_code #(N)
  ( input logic [ N-1:0] x,
    output logic [2**N-2:0] y ) ;
  always_comb begin
    y = '0 ;
    for ( int i=0 ; i<2**N-2 ; i++ )
      y[i] = i < x ;
  end
endmodule

module thermometer_code_tb ;
  logic [2:0] x = 3'b110 ;
  logic [6:0] y ;
  thermometer_code #(3) t0 (*.*) ;
  initial begin
    #1 ;
    $displayb(y) ;
    $finish ;
  end
endmodule
```

The output of the testbench is:

```
# vsim -batch thermometer_code_tb -do "run -all"
...
# Loading work.thermometer_code_tb
# Loading work.thermometer_code
#
# run -all
# 0111111
```

4.48 and 4.49 The two modules are:

```
module code1(input logic clk, a, b, c,
              output logic y);
  logic x;
  always_ff @(posedge clk) begin
    x <= a & b;
    y <= x | c;
  end
endmodule


module code2 (input logic a, b, c, clk,
              output logic y);
  logic x;
  always_ff @(posedge clk) begin
    y <= x | c;
    x <= a & b;
  end
endmodule
```

The only difference between code1 and code2 is the order of the two assignments in the always_ff block.

When non-blocking assignments are used, the values of x and y don't change until the end of the always block. The schematics are the same since the values of x and y used are the values at the flip-flop outputs.

When blocking assignments are used, the values are updated immediately so in code1 the value of x used in the second assignment is the and result, not the flip-flop output while the behaviour code2 remains unchanged since the value of x is used before it is assignment to.

 The generated schematics are as follows (the 'b' suffix indicates blocking assignments):



4.27 An example of a module and testbench for a JK flip-flop is:

```

module jkff ( input logic j, k, clk,
               output logic q ) ;
  always@(posedge clk)
    case({j,k})
      2'b00: q <= q ;
      2'b01: q <= '0 ;
      2'b10: q <= '1 ;
      2'b11: q <= ~q ;
    endcase
endmodule

module jkff_tb ;
  logic j, k, clk, q;
  jkff j0 (.*) ;

  initial begin
    for ( logic [3:0] i=4'b0100 ;
          i<4'b1101 ; i++ )
      #1us {j,k,clk} = i[2:0] ;
    $stop ;
  end
endmodule

```

For which the simulation output is shown in Figure 1.

 


Figure 1: JK flip-flop simulation results.