

Solutions to Final Exam


Question 1

For the following declarations in a System Verilog module:

```
logic a = '1 ;
logic [7:0] b = 8'ha6 ;
logic [1:0][3:0] c = '{4'b0000, 4'b1001 };
```


the simulation output below shows sizes and values of the following expressions:

```
b==?8'bxxxx0110: bits: 1 val: 0000 0001
signed'(b) >>> 1: bits: 8 val: 1101 0011
{b[7:1],a}: bits: 8 val: 1010 0111
b[7:4]: bits: 4 val: 0000 1010
{2{c}}: bits: 16 val: 0000 1001
b+1'b1: bits: 8 val: 1010 0111
a ? b : c: bits: 8 val: 1010 0110
```

 

Question 3

The following schematic:

 

Question 2

The following code:

```
module examtb ( output logic ca, cb ) ;

initial begin
    ca = '1 ;
    cb = '1 ;

#30ns cb = '0 ;
#10ns ca = '0 ;

forever begin
    #10ns cb = ~cb ;
    #10ns ca = ~ca ;
end

end

endmodule
```

generates the required waveforms:

implements the following System Verilog module:

```
module mksum
( output logic [15:0] c,
  input logic reset, clk ) ;

logic [15:0] a, a_next, b, b_next ;

always@(posedge clk) begin
    a <= a_next ;
    b <= b_next ;
    c <= a_next + b_next ;
end

always_comb begin
    if ( reset ) begin
        a_next = '0 ;
        b_next = '0 ;
    end else begin
        a_next = a + 16'd113 ;
        b_next = b + 16'd127 ;
    end
end
```

```


    end
end

endmodule

```

Question 4

The following state transition diagram:

 

can be implemented by the following System Verilog module:

```

// ELEX 7660 201710 Final Exam Question 4

module pulsegen (
    input logic pb,
    output logic pulse,
    input logic clk, reset ) ;

    typedef enum logic [1:0] { S0, S1, S2 }
        state_t ;
    state_t state, next_state ;

    logic pulse_next ;

    // your code goes here

    always_comb begin

        next_state = state ;

        if ( reset )
            next_state = S0 ;
        else
            case(state)
                S0: if ( pb == 0 )
                    next_state = S1 ;
                S1: next_state = S2 ;
                S2: if ( pb == 1 )
                    next_state = S0 ;
            endcase
    end

    always_comb begin
        if ( next_state == S1 )
            pulse_next = '1 ;
        else
            pulse_next = '0 ;
    end

```

```

    end

    always_ff@(posedge clk) begin
        state <= next_state ;
        pulse <= pulse_next ;
    end

endmodule

module examq4 ;
    logic pb, pulse, clk, reset ;
    pulsegen p0 ( pb, pulse, clk, reset ) ;
    // clock and reset
    initial begin
        reset = '1 ;
        clk = '0 ; #500ns ;
        clk = '1 ; #500ns ;
        reset = '0 ;
        forever begin
            clk = '0 ; #500ns ;
            clk = '1 ; #500ns ;
        end
    end

    // pushbutton
    initial begin
        $dumpfile("examq4.vcd") ;
        $dumpvars ;
        pb = '1 ;
        #2us pb = '0 ;
        #2us pb = '1 ;
        #2us $finish ;
    end
endmodule

```

with the simulation results shown in Figure 1.

Question 5

The following timing specifications are found in the datasheet for an audio codec IC:

Control Interface Timing (3-wire Serial: AK4951EG)						
	tCCK	200	-	-	-	ns
CCLK Period	tCCKL	80	-	-	-	ns
CCLK Pulse Width Low	tCCKH	80	-	-	-	ns
Pulse Width High						
CDTIO Setup Time	tCDS	40	-	-	-	ns
CDTIO Hold Time	tCDH	40	-	-	-	ns
CSN "H" Time	tCSW	150	-	-	-	ns
CSN Edge to CCLK "↑"	tCSS	50	-	-	-	ns
CCLK "↑" to CSN Edge	tCSH	50	-	-	-	ns
CCLK "↓" to CDTIO (at Read Command)	tDCD	-	-	-	70	ns
CSN "↑" to CDTIO (Hi-Z) (at Read Command)	tCCZ	-	-	-	70	ns



 


Figure 1: Question 4 testbench results.

 y The timing diagram for a read cycle is:



The timing diagram for a write cycle is:

 

The signal directions are:

Signal	Direction
CSN	input
CCLK	input
CDTIO	input (during write cycles)
CDTIO	output (during read cycles)

- (a) Specifications whose time ends at an input (I) are requirements, those ending at an output (O) are “guaranteed responses.”

specification	Measured to (I/O)	Requirement (R) or Guaranteed (G)
tCCK	CCLK (I)	R
tCDS	CCLK (I)	R
tCDH	CDTIO (I)	R
tDDC	CDTIO (O)	G

- (b) The maximum clock (CCLK) frequency is given by the inverse of the minimum clock period (200ns) or 5 MHz.

- (c) During a write cycle the data (CDTIO) must be valid tCDS (40 ns, CDTIO setup time) before the rising edge of the clock. If the clock period is 1 μ s (1000 ns), then the maximum delay between the previous rising clock edge and CDTIO being valid is $1000-40=960$ ns.
- (d) The minimum delay between the rising edge of CCLK and CDTIO being invalid is tCDH which is 40 ns.