

ELEX 7660 : Digital System Design
Term 201710

MIDTERM EXAMINATION - PART 2
1:30 PM – 2:20 PM
February 28, 2017

This exam has two (2) questions on five (5) pages. The marks for each question are as indicated. There are a total of 18 marks. Answer all questions. Write your answers and all rough work in this paper and nowhere else. Show your work. Books and notes are allowed. No electronic devices other than calculators are allowed.

This exam paper is for:

Exam 1 A00123456

Each exam is equally difficult.
Answer your own exam.

Do not start until you are told to do so.

Name: _____


BCIT ID: _____

Signature: _____

Question	Mark	Max.
1		9
2		9
Total		18

 
Question 1 (9 marks)

Write a System Verilog module that models the schematic shown below on the facing page. Use logic signal types throughout. Include all code from module to endmodule. Where the order of declarations or statements is not significant you may use any order.



Question 2 (9 marks)

Using the following symbols:

 

draw a schematic for the following Verilog module on the facing page. Label the inputs and outputs. Indicate the bus width if it's more than 1 bit.

```
module mkmini
( output logic [15:0] a,
  input logic [15:0] d,
  output logic [15:0] mini,
  input logic reset, clk );

  logic [15:0] a_next ;
  logic [15:0] mini_next ;

  always@(posedge clk) begin
    mini <= mini_next ;
    a <= a_next ;
  end

  always_comb begin
    if ( reset )
      mini_next = '1 ;
    else
      mini_next = d < mini ? d : mini ;

    if ( reset )
      a_next = '0 ;
    else
      a_next = a + 1'd1 ;
  end
endmodule
```


- This page intentionally left blank. -

ELEX 7660 : Digital System Design
Term 201710

MIDTERM EXAMINATION - PART 2
1:30 PM – 2:20 PM
February 28, 2017

This exam has two (2) questions on five (5) pages. The marks for each question are as indicated. There are a total of 18 marks. Answer all questions. Write your answers and all rough work in this paper and nowhere else. Show your work. Books and notes are allowed. No electronic devices other than calculators are allowed.

This exam paper is for:

Exam 2 A00123456

Each exam is equally difficult.
Answer your own exam.

Do not start until you are told to do so.

Name: _____


BCIT ID: _____

Signature: _____

Question	Mark	Max.
1		9
2		9
Total		18

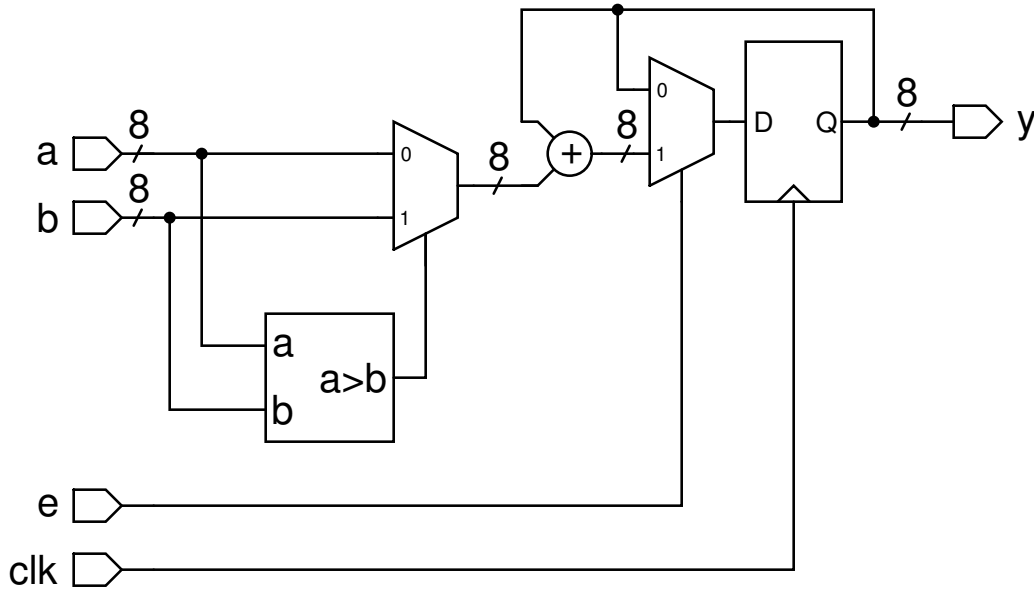
Question 1 (9 marks)

Write a System Verilog module that models the schematic shown below on the facing page. Use logic signal types throughout. Include all code from module to endmodule. Where the order of declarations or statements is not significant you may use any order.



Question 2 (9 marks)

Using the following symbols:

 

draw a schematic for the following Verilog module on the facing page. Label the inputs and outputs. Indicate the bus width if it's more than 1 bit.

```
module mksum
( output logic [15:0] a,
  input logic [15:0] d,
  output logic [15:0] sum,
  input logic reset, clk ) ;

  logic [15:0] a_next ;
  logic [15:0] sum_next ;

  always@(posedge clk) begin
    sum <= sum_next ;
    a <= a_next ;
  end

  always_comb begin
    sum_next = reset ? '0 : sum + d ;

    if ( reset )
      a_next = '0 ;
    else
      a_next = a + 1'd1 ;
    end

endmodule
```


- This page intentionally left blank. -