

## Solutions to Midterm Exam

### Question 1

The two versions of this question used the same expressions arranged in different orders. The following code computes the size and value of each expression:

```
// solutions for midterm exam question 1
module midterm ;

    logic signed [7:0] a = 8'h80 ;
    logic [3:0] b [3:0] =
        '{ 4'bxxxx, 4'h1, 4'd2, 4'b0011 } ;
    logic [3:0] c = '1 ;

`define ans(expr) \
    $display("%16s: bits: %2d value: %8b", \
        "expr", $bits(expr), expr) ;

    initial begin
        `ans( a+1 ) ;
        `ans( b[0] ==? 4'bxxx1 ) ;
        `ans( a[0] ? 0 : 2 ) ;
        `ans( {2{a[7:4]}} ) ;
        `ans( &c ) ;
        `ans( a >>> 1 ) ;
        `ans( b[1] ) ;
        `ans( c && a ) ;
        `ans( b[2]==c ) ;
    end

endmodule
```

and the output is:

```

a+1: bits: 32 value: 1...10000001
b[0] ==? 4'bxxx1: bits: 1 value: 00000001
a[0] ? 0 : 2: bits: 32 value: 00000010
{2{a[7:4]}}: bits: 8 value: 10001000
&c: bits: 1 value: 00000001
a >>> 1: bits: 8 value: 11000000
b[1]: bits: 4 value: 00000010
c && a: bits: 1 value: 00000001
b[2]==c: bits: 1 value: 00000000
```

### Question 2

- There were two versions of the question. In both the clock signal is initialized to 0 and the simulation runs for four delays of 1  $\mu$ s (4  $\mu$ s total). There are two rising clock edges (at 1 and 3  $\mu$ s).
- In the first version of the question x is initialized to 1 and is incremented by 2 on each rising clock

edge; in the second it is initialized to 0 and incremented by 1. So x takes on three values – the initial value and one after each clock edge – and the values of x are 1, 3, 5 (first version) or 0, 1, 2 (second version).


- The `$display()` function in the `always_ff` block executes immediately after a non-blocking assignment so the value of x will not have been updated yet. So the first version prints:

```
# 1
# 3
```

while the second version prints:

```
# 0
# 1
```

 - The `always_comb` block executes and updates y whenever x changes. The value of y is set to x+1 if the LS bit of x is set (x is odd) else to zero. So in the first version y is set to (2,4,6); in the second it is set to (1,0,3) as shown below:



### Question 3


To convert a schematic to HDL, we:

- list each input or output in a module statement
- assign to each register or flip-flop output using a non-blocking assignment in an `always_ff` block

- model each multiplexer as an if/else in an always\_comb block, using local signal names as necessary
- model combination logic blocks as operators

It's often possible to simplify the solution using continuous assign statements or the ternary operator.

For the first schematic:

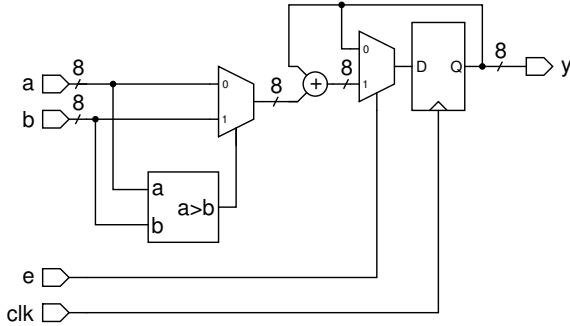

examples of concise and more verbose System Verilog solutions are:

```

module midterm3a
  ( input logic [7:0] a, b,
    output logic [7:0] y,
    input logic e, clk );

`ifdef simple

  always_ff@(posedge clk)
    y <= e ? y + ( a>b? b : a ) : y ;

`else

  logic [7:0] y_next, y_sum ;

  always_ff@(posedge clk)
    y <= y_next ;

  always_comb
    if ( e )
      y_next = y_sum ;
    else
      y_next = y ;


  always_comb
    if ( a > b )
      y_sum = b ;
    else
      y_sum = a ;

`endif

endmodule

```

and for the second schematic:

 

examples of the System Verilog code are:

```

module midterm3b
  ( input logic [7:0] a, b,
    output logic [7:0] y,
    input logic s, e, clk );

`ifdef simple

  always_ff@(posedge clk)
    y <= e ? ( s ? a-b : a+b ) : y ;

`else

  logic [7:0] y_next, y_sumdiff ;

  always_ff@(posedge clk)
    y <= y_next ;

  always_comb
    if ( e )
      y_next = y_sumdiff ;
    else
      y_next = y ;

  always_comb
    if ( s )
      y_sumdiff = a - b ;
    else
      y_sumdiff = a + b ;

`endif

endmodule

```

---

### Question 4

---

There were two System Verilog modules. Drawing the schematic involves drawing:

- an I/O connector for each input or output in the module statement
- a register or flip-flop for each always\_ff block

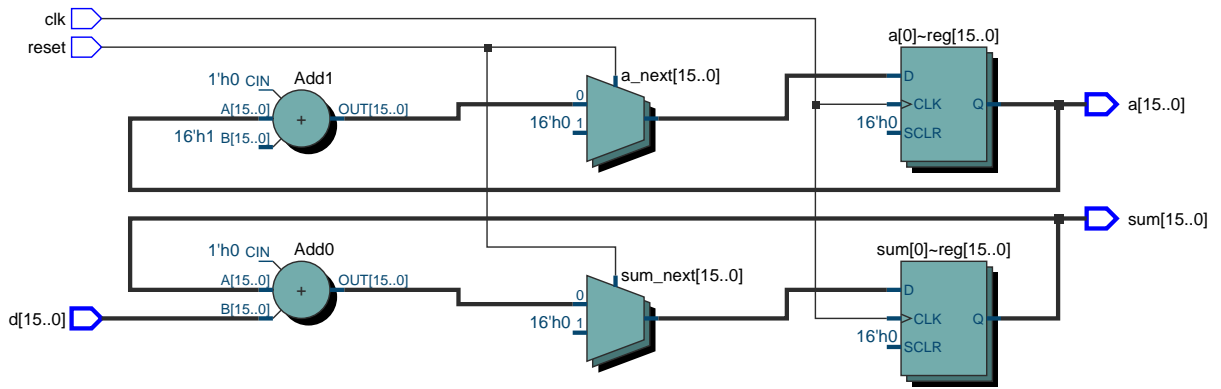


Figure 1: mksum schematic.

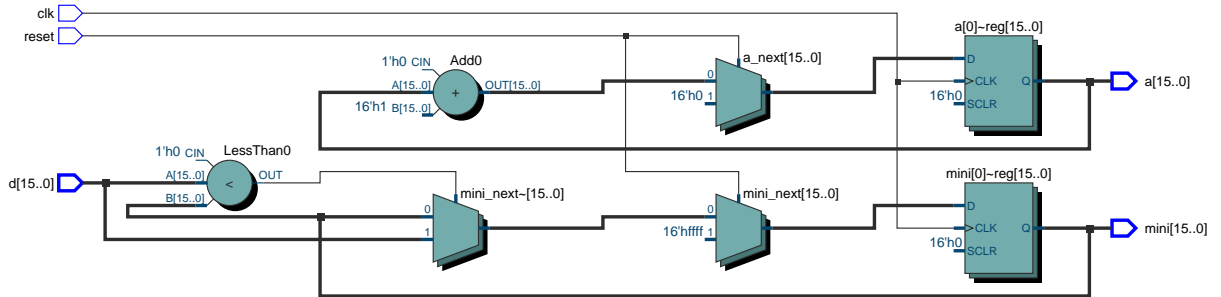


Figure 2: mkmini schematic.

- a multiplexer for each if/else or ternary operator
- a combinational logic block for each operator in an expression

Figure 1 shows the Quartus-generated schematic for the `mksum` module and Figure 2 shows the Quartus-generated schematic for the `mkmini` module.