
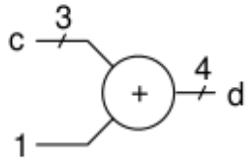


assign z = x != y;

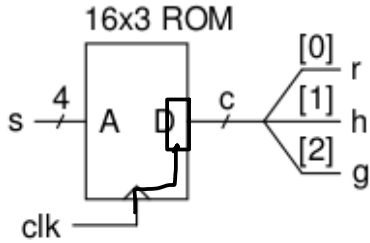


logic [3:0] d
[2:0] c

d = c + 1'd1;



always_ff @ (posedge clk)

c <= rom[s];

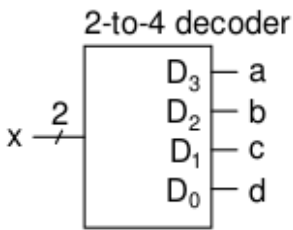

r = c[0];
h = c[1];
g = c[2];

	D ₃	D ₂	D ₁	D ₀
00	0	0	0	1
01	0	0	1	0
10	0	1	0	0
11	1	0	0	0

a = '0; d = '0;

b = '0

c = '0

case (x)

2'b00: a = '1;

2'b01: c = '1;

2'b10: b = '1;

2'b11: a = '1;

endcase

D = 4'b0001;

a = D[3]
b = D[2]

a = (b = (c = (d = 0)))

logic [3:0] D




{a, b, c, d} = 4'b0001;

{a, b, c, d} = 1'b1 << x;

logic [3:0] D [1:0] = {4'b0001, ...}

if (x == 2'b00)
{a, b}

{a, b, c, d} = D[x];

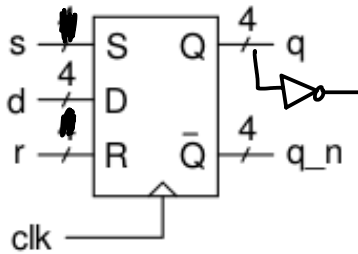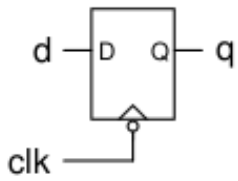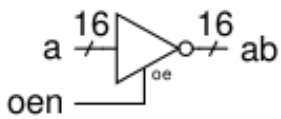


S

$$ab = 16'bz;$$

$$ab = oen ? \sim a : 'z;$$
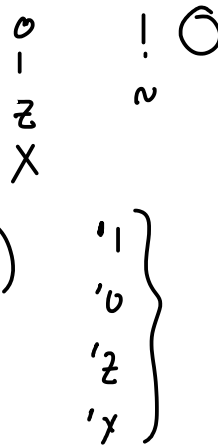
```
always_ff @(negedge clk)
  q <= d;
```



```
always_ff @(posedge clk)
```

```
  if (s)
    q <= '1;
  else if (r)
    q <= '0;
  else
    q <= d;
```

```
  assign q_n = ~q; ???
```

```
always_comb begin
```

```
  q_next = s ? '1 : r ? '0 : d;
```

```
  q_n_next = ~q_next;
```


```
end
```

```
always_ff @(posedge clk)
```

```
  q <= q_next;
```

```
  q_n <= q_n_next;
```

```
end
```

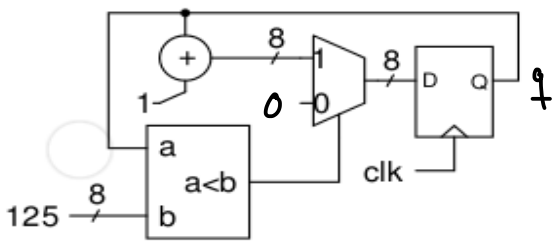


```

always-comb
q_next = q < 125 ? q + 1'b1 : '0;

always_ff (@ posedge clk)
q <= q_next;

```

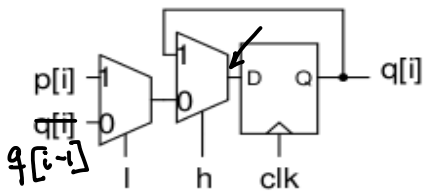


```


-----
if (h)
    d[i] = q[i];
else if (1)
    d[i] = p[i];
else
    d[i] = q[i-1];


-----
always_ff (@
    q[i] <= d[i]
)

```

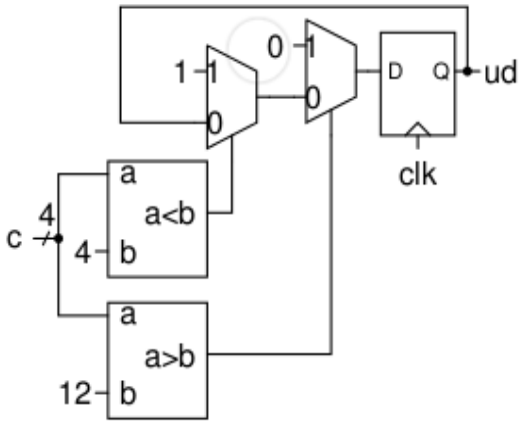

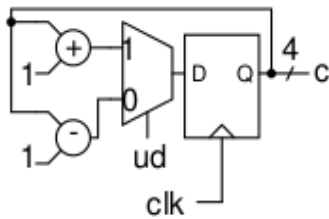(this is [almost?] the example from lecture 1)



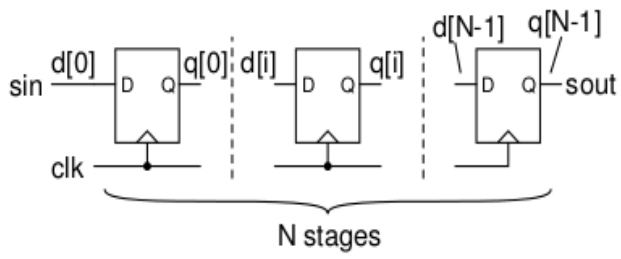

```

module test (input logic sin, clk, output logic sout ) ;
parameter N = 31 ;
logic q[N-1:0] ;

always_ff@(posedge clk) begin
    q[0] <= sin ;
    for ( int i=1 ; i<N ; i++ ) begin
        q[i] <= q[i-1] ;
    end
end

assign sout = q[N-1] ;

endmodule

```