

Assignment 1

Due Tuesday, February 13. Submit your assignment using the appropriate dropbox on the course web site. Assignments submitted after the solutions are made available will be given a mark of zero.

Question 1

This questions asks you to explore different ways of describing combinational logic functions in System Verilog.

A half adder has two one-bit inputs and two one-bit outputs: the sum and the carry. It can be described by the following truth table:

a	b	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

where a and b are the inputs and sum and carry the outputs.

Write a System Verilog module that computes the sum and carry in six different ways:

- using only logic operators (&, |, ^)
- using only ternary operators (?:)
- using only if/else statements
- using only a case statement
- using only concatenation ({,}), addition (+) and bit subscript (slicing) ([:]) operators
- using only initialized array(s), concatenation ({,}) and the indexing operator ([])

Question 2

You can implement multiplication as addition of shifted versions of a multiplicand. The additions are controlled by the bits of the multiplier. For example, to multiply $a=4'b1010$ (10) by $b=4'b011$ (3) we would add $c = (a \ll 0) * b[0] + (a \ll 1) * b[1] + (a \ll 2) * b[2] = 1010 + 10100 + 000000 = 11110$ (30).

Complete the following System Verilog 8×8 multiplier module. Use a for-loop so your design has only combinational logic.

```
module mul8 ( input logic [7:0] a,
             input logic [7:0] b,
             output logic [15:0] c );

    always_comb begin
        // your code here
    end

endmodule

module mul8_tb ;

    logic [15:0] res ;

    mul8 m0 (8'd12, 8'd34, res ) ;

    initial begin
        #1 $display ( "The product is %d\n", res ) ;
        $finish ;
    end


endmodule
```

Test you design using the last four digits of your BCIT ID as the two two-digit test values. For example, if your BCIT ID number is A00123456 then your example should multiply 34 and 56.

Your answer should include your code and a screen capture of the transcript window showing the correct result.

 Question 3

Design a controller called asg1 with the following interface:



bits	name	in/out	notes
1	write	in	active-high
32	data	in	
1	clk	in	
32	address	out	
1	valid	out	active-high

The controller operates as follows:

The outputs change only on the rising edge of `clk`. When `write` is asserted `address` is set to 0, the value on the `data` input is stored, and `valid` is asserted. On each subsequent clock pulse the `address` output increases by 1 until it reaches the value stored. `valid` is de-asserted on the next clock cycle.

- Write the state transition table.
- Draw the state transition diagram.
- Write a synthesizable System Verilog description. Your design should use only one `always_comb` block and one `always_ff` block.
- Test your design using the testbench supplied on the course web site.

The simulation results are shown above.