

Introduction to Digital Design with Verilog HDL

Exercise 1: What changes would result in a 3-input OR gate?


```
// AND gate in Verilog

module ex1 ( input logic a, b, c,
             output logic y ) ;

    assign y = a & b ; a | b | c ;

endmodule
```

Exercise 2: What schematic would you expect if the statement was `assign y = a ? b : c ;`?

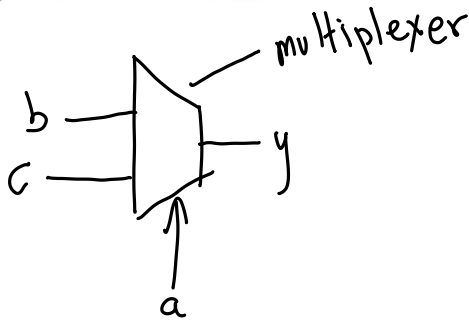

Exercise 3: What change might produce a 4-bit 4-to-1 multiplexer controlled by a 2-bit sel input?

```
module ex3 (input logic [1:0] sel,
            input logic [3:0] a, b, c, d
            output logic [3:0] y) ;
```

```
    always_comb begin
        if ( sel ) y <= a ;
        else y <= b ;
    end
```

```
endmodule
```

```
    if (sel == 2'b00)
        y = a
    ....
```

Exercise 4: If the signal `i` is declared as `logic [2:0] i;`, what is the 'width' of `i`? If `i` has the value 6 (decimal), what is the value of `i[2]`? Of `i[0]`?

*i is 3 bits
(2...0)*

6 = 110
i[2] = 1 *i[0] = 0*

Exercise 5: What are the values in decimal of the constants in the code above?


0: `d = 8'hc0 ;` *→ 192*
 1: `d = 8'b1111_1001 ;` *→ F9 = 249*
 2: `d = 'ha4 ;` *A = 164*
 default: `d = 176 ;` *176*

Exercise 6: What is the output in binary when the input is `a=2'b10` *→ 2₁₀*

A4 = 1010 0100

Exercise 7: Which ports are mapped by `.*` in the instantiation of `ex5`?

`ex5 ex5_0 (.*, .x(count)) ;`

 

Exercise 8: Write the module declaration for ex7.

```
ex7 ex7_0 ( .n(count), .seg ) ;  
  
    output logic [7:0] seg ) ;  
  
logic [3:0] count ;
```

in ex7: input [3:0] n
out put [7:0] seg.

```
module ex7 ( input [3:0] n,  
            output [7:0] seg ) ;
```

Exercise 9: Where in the code is the Device Under Test (DUT) instantiated?

```
ex5 ex5_0 (.*);
```

↑ module name
↑ instance name
↑ port connections