

RF Design - Noise

Exercise 1: What is the noise figure of a 6 dB attenuator?

$$F = S_i / S_o = 4 \text{ (+6 dB)}$$

$$10^{\frac{6}{10}} = \frac{1}{4}$$

$$\frac{W}{H_z} \cdot H_z \Rightarrow W$$

$$S_i = 1W \quad \square \quad S_o = \frac{1}{4}$$

$$\text{dBm} - \text{dBHz} + \text{dBHz} \Rightarrow \text{dBm}$$

$$\text{"dBm/Hz"} = \text{dBHz}$$

$$B(\text{dBHz}) = 10 \log(B(\text{Hz}))$$

Exercise 2: What are the minimum possible values of T_e and F ?

$$T_e (\text{min}) = 0 \text{ K}$$

$$F (\text{min}) = 1 + \frac{T_e}{T_0} = 1 \text{ (0 dB)}$$

Exercise 3: The datasheet for a low-noise amplifier (LNA) specifies a noise figure of 2 dB. What is the noise temperature T_e ?

$$F = 2 \text{ dB} = 10^{\frac{2}{10}} = 1.58$$

$$F = 1 + \frac{T_e}{T_0}$$

$$T_e = (F - 1) T_0$$

$$= (1.58 - 1) T_0$$

$$= 0.58 \cdot 290 = 170 \text{ K}$$

Exercise 4: An LNA with a noise figure of 0.3 dB receives a signal with an SNR of 6 dB. What is the output SNR?

$$F = \frac{SNR_{in}}{SNR_{out}}$$

$$SNR_{out} = SNR_{in} \cdot F$$

$$= SNR_{in} (dB) - F (dB)$$

$$= 6 - 0.3 = 5.7 \text{ dB}$$

Exercise 5: A noise source with an ENR of 15 dB is connected to an LNA. The noise PSD at the output of the LNA is measured as -152 dBm/Hz and with the noise source on and -165.2 dBm/Hz with it off. Assuming the spectrum analyzer adds negligible noise and the "off" noise source temperature is 0 K, what are T_e and F ? Do not confuse mW and dBm.

$$F_{dB} = ENR_{dB} - 10 \log_{10}(Y - 1)$$

$$-152.0 \text{ dBm/Hz}$$


$$-165.2 \text{ dBm/Hz}$$

$$Y = 13.2 \text{ dB}$$

$$= 20.9$$

$$F_{dB} = 15 - 10 \log_{10}(20.9 - 1)$$

$$= 2.01 \text{ dB}$$

$$= 1.59$$


$$F = 1 + \frac{T_e}{T_0}$$

$$T_e = T_0 (F - 1) = 290 (0.59)$$

$$= 171 \text{ K}$$

Exercise 6: A What is the system noise figure of a receiver that consists of a 10 dB amplifier with 3 dB noise figure followed by a mixer with a 6 dB loss and an IF amplifier with a 20dB gain and a noise figure of 10 dB?

$$F = \frac{F_1}{G_1} + \frac{F_2}{G_1 G_2} + \frac{F_3}{G_1 G_2 G_3} \quad (\text{dB})$$

$$= 2 + 4 + 10 \quad (\text{linear})$$

$$G = \frac{G_1}{G_1} + \frac{G_2}{G_1} + \frac{G_3}{G_1 G_2} \quad (\text{dB})$$

$$10 \quad \frac{1}{4} \quad 100 \quad (\text{linear})$$

$$F = 2 + \frac{4-1}{10} + \frac{10-1}{10 \cdot \frac{1}{4}} = 2 + 0.3 + 3.6 = 5.9$$

$$= 3.9 \text{ dB}$$